



## Lecture – 9


# Programmable Logic Devices

### Lesson Outcomes

- After completing this lecture, students will be able to
- Describe the difference between an PAL and GAL
  - Explain the principle of operation of PAL and PLA
  - Explain the difference of SPLD and CPLD
  - Apply PAL and PLA for CPLDs, for example, PROM and FPGA



# Digital Systems Family Tree

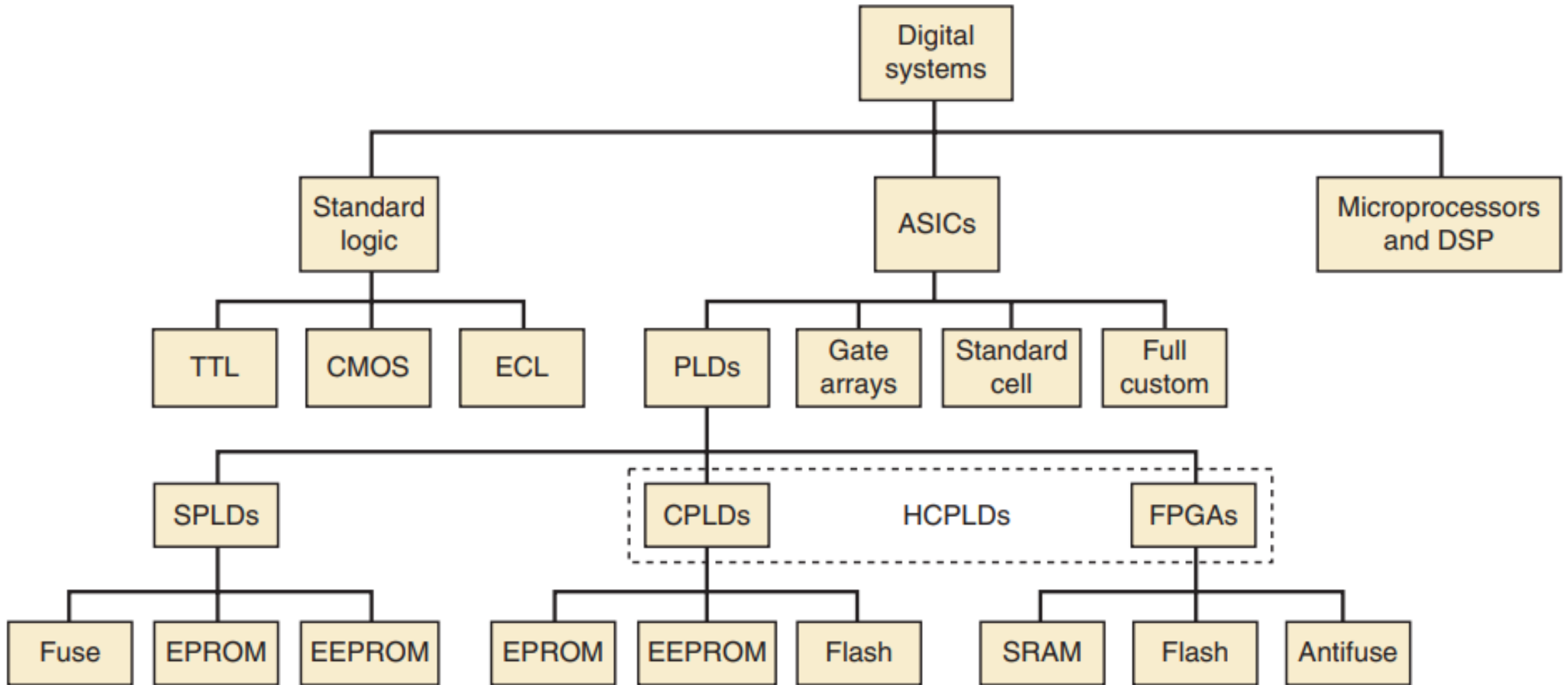





# Digital Systems Family Tree

TTL : Transistor Transistor Logic  
CMOS: Complementary Metal-Oxide Semiconductor  
ECL : Emitter Coupled Logic  
SPLD : Simple Programmable Logic Device  
CPLD : Complex Programmable Logic Device  
HCPLD: High Capacity Programmable Logic Device  
PAL : Programmable Array Logic  
GAL : Generic Array Logic  
PLA : Programable Logic Array  
FPGA : Field Programable Gate Array  
EPROM: Erasable Programmable Read Only Memory  
EEPROM: Electrically Erasable Programmable Read Only Memory  
SRAM: Static Random Access Memory
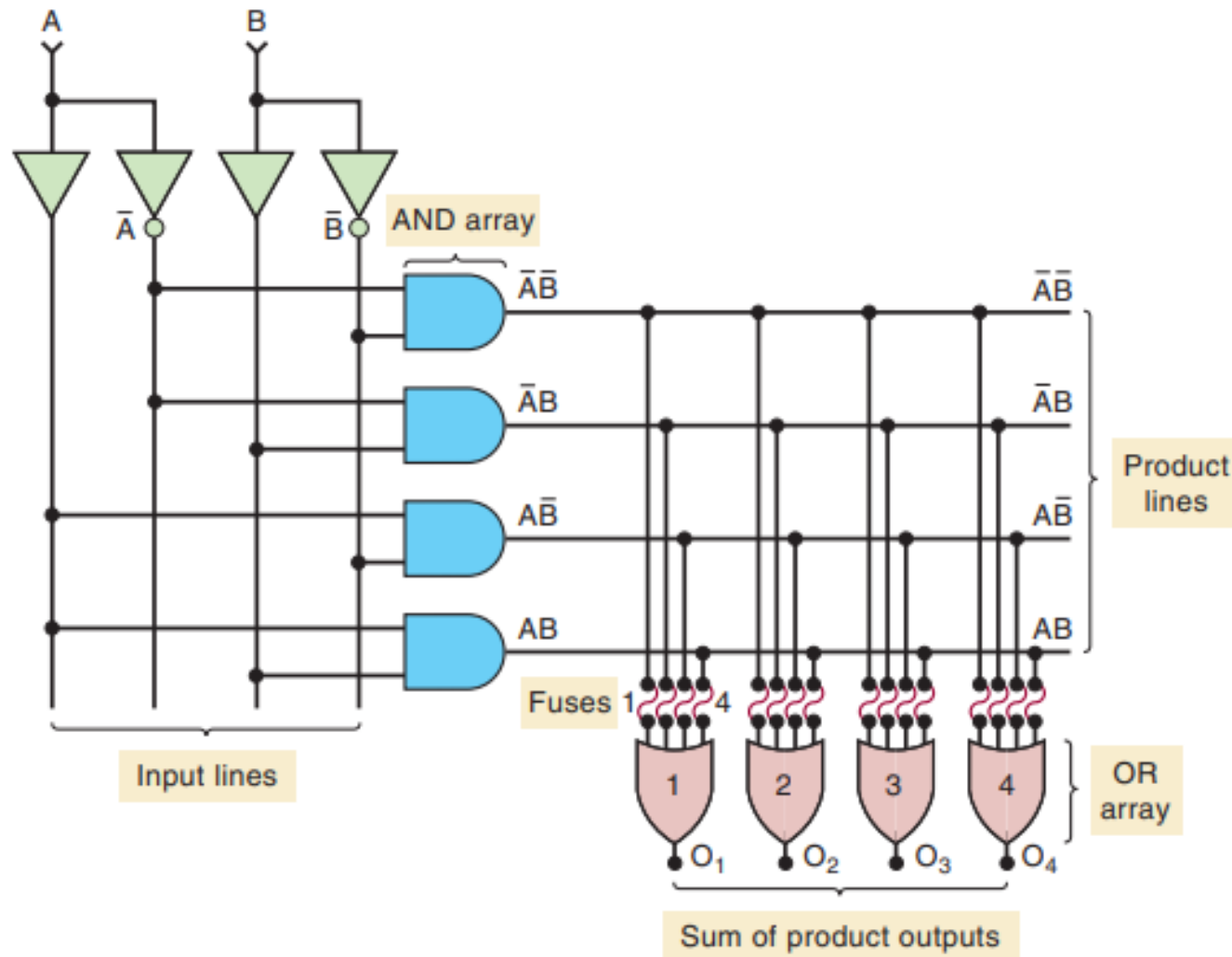
# PLDs (Programmable Logic Devices) – symbology




Programmable Logic Devices - example

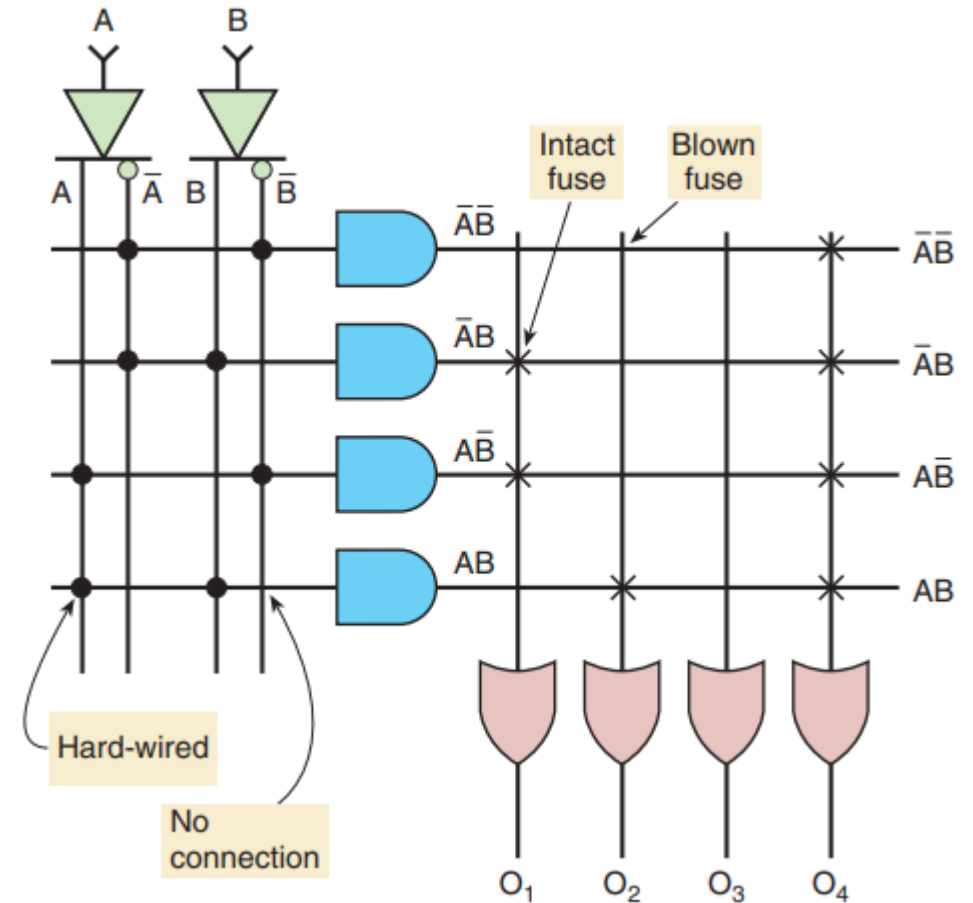

Simplified PLD Symbology


# PLAs – Programmable Logic Arrays

 


## EXAMPLE 10-1

Show how a PAL is programmed for the following 3-variable logic function:  $X = A\bar{B}C + \bar{A}B\bar{C} + \bar{A}\bar{B} + AC$


### Solution

 

# PAL AND PLA: basic difference

 


(a) PAL-type array

 

(b) PLA-type array

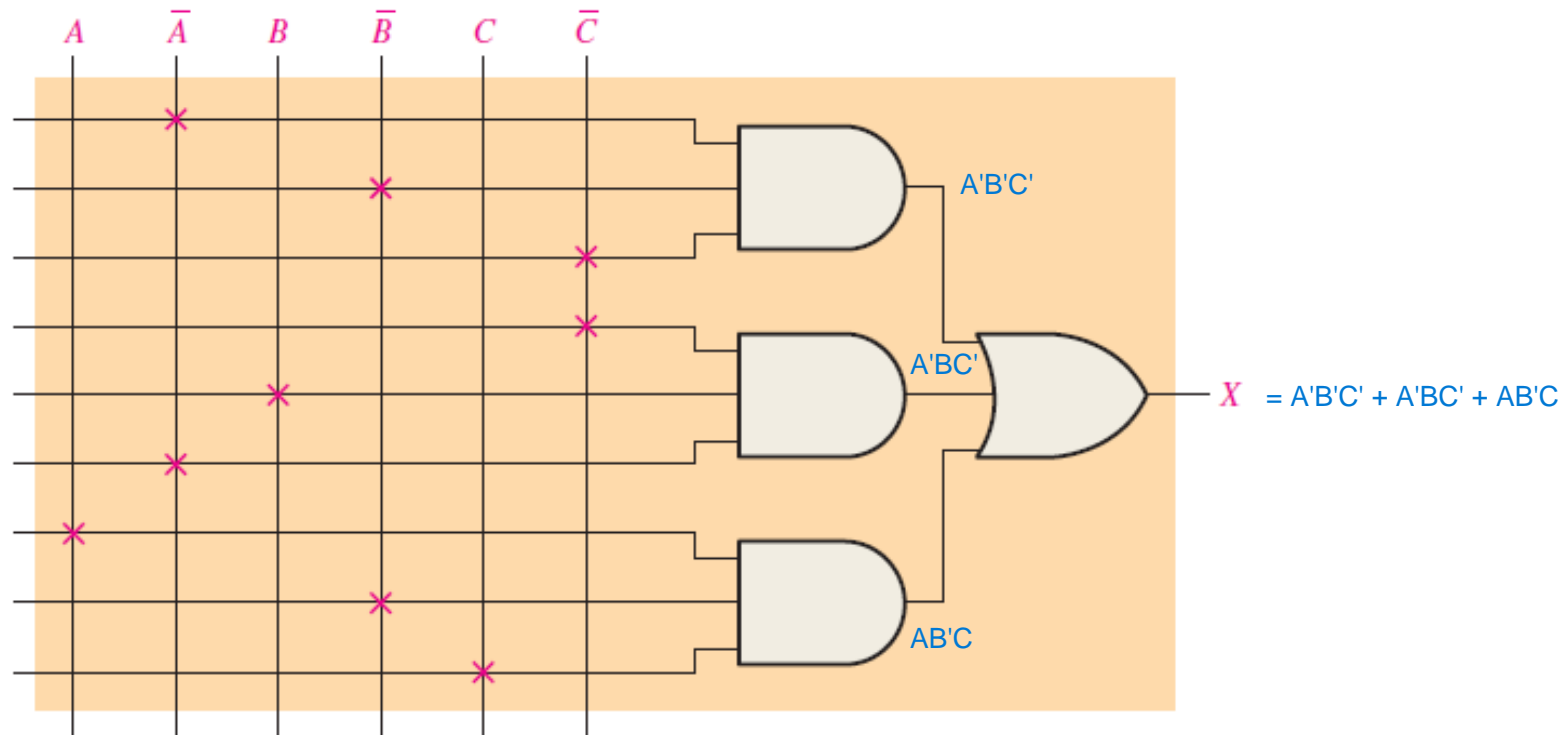**PROBLEM.** Determine the Boolean output expression for the simple PAL array shown in Figure. The Xs represent connected links.






# Example

**PROBLEM.** Show how the PAL-type array in Figure should be programmed to implement each of the following SOP expressions. Use an X to indicate a connected link.

(a)  $Y = A\bar{B}C + \bar{A}B\bar{C} + ABC$

 (b)  $Y = A\bar{B}C + \bar{A}\bar{B}C + \bar{A}BC$




# Example

**PROBLEM.** Determine the output of the array in Figure. The Xs represent connected links.

 
**PROBLEM.** Modify the array in Figure to produce an output


$$X = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + ABC + A\overline{B}C$$




# Example

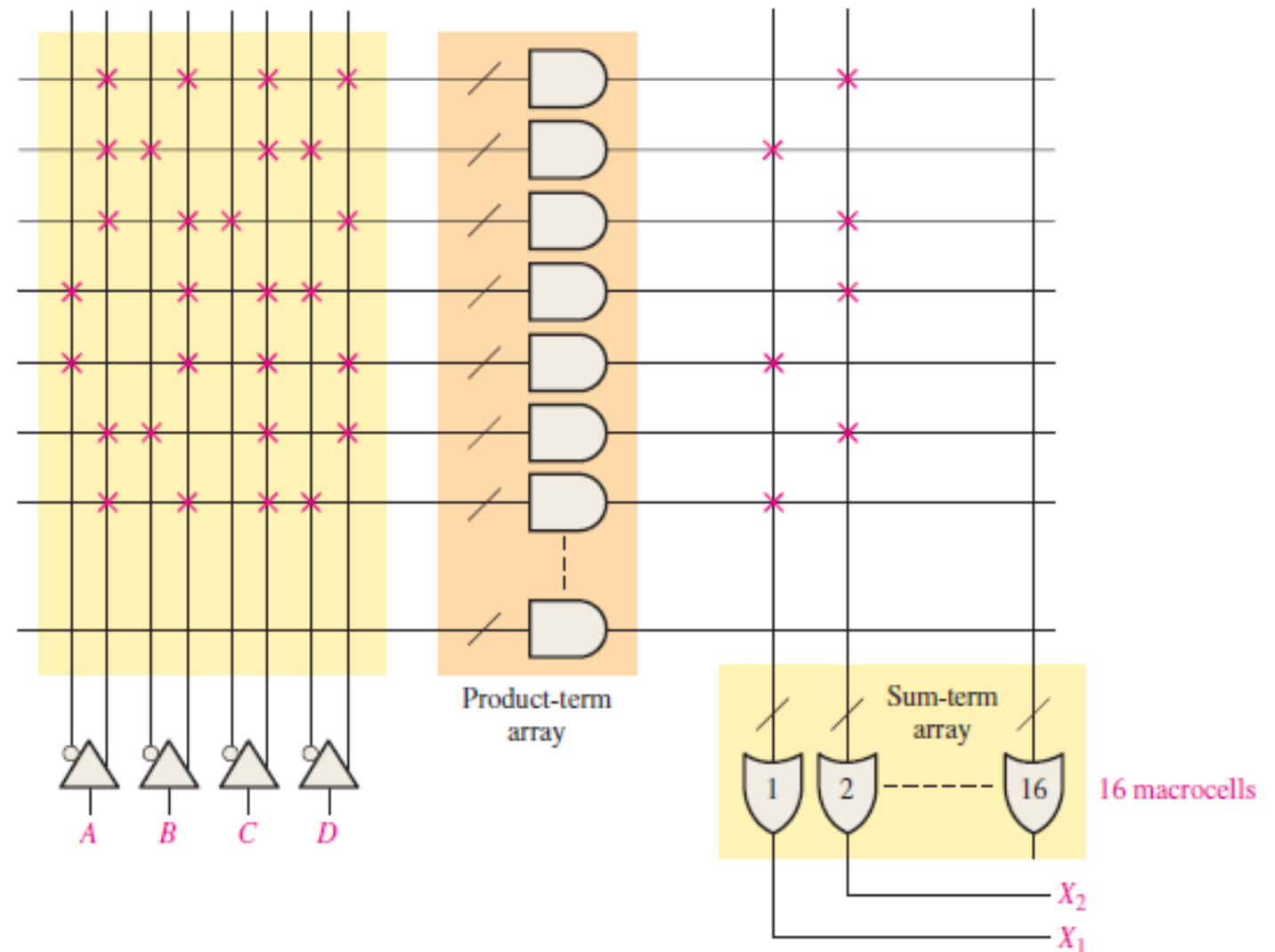**PROBLEM.** Determine the output expressions for  $X_1$  and  $X_2$  from macrocells 1 and 2 in Figure.



 

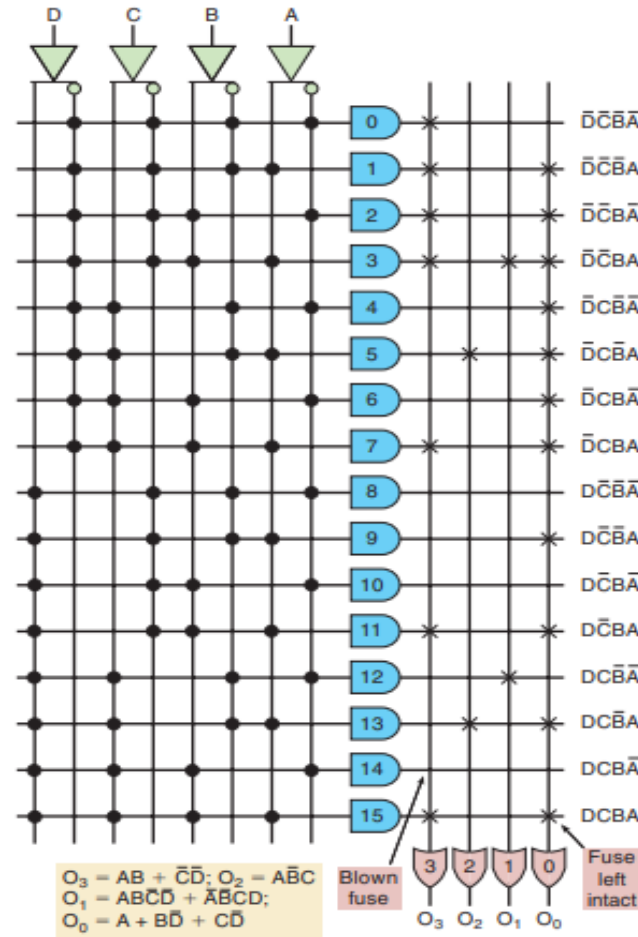(a) PROM architecture makes it suitable for PLDs




(b) fuses are blown to program outputs for given functions


D	C	B	A	$O_3$
0	0	0	0	1 → $\bar{D}\bar{C}\bar{B}\bar{A}$
0	0	0	1	1 → $\bar{D}\bar{C}\bar{B}A$
0	0	1	0	1 → $\bar{D}\bar{C}B\bar{A}$
0	0	1	1	1 → $\bar{D}\bar{C}BA$
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1 → $\bar{D}CBA$
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1 → $D\bar{C}BA$
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1 → $DCBA$

A PROM used to generate a logic function on  $O_3$ .

# PROM – Programmable Logic Array

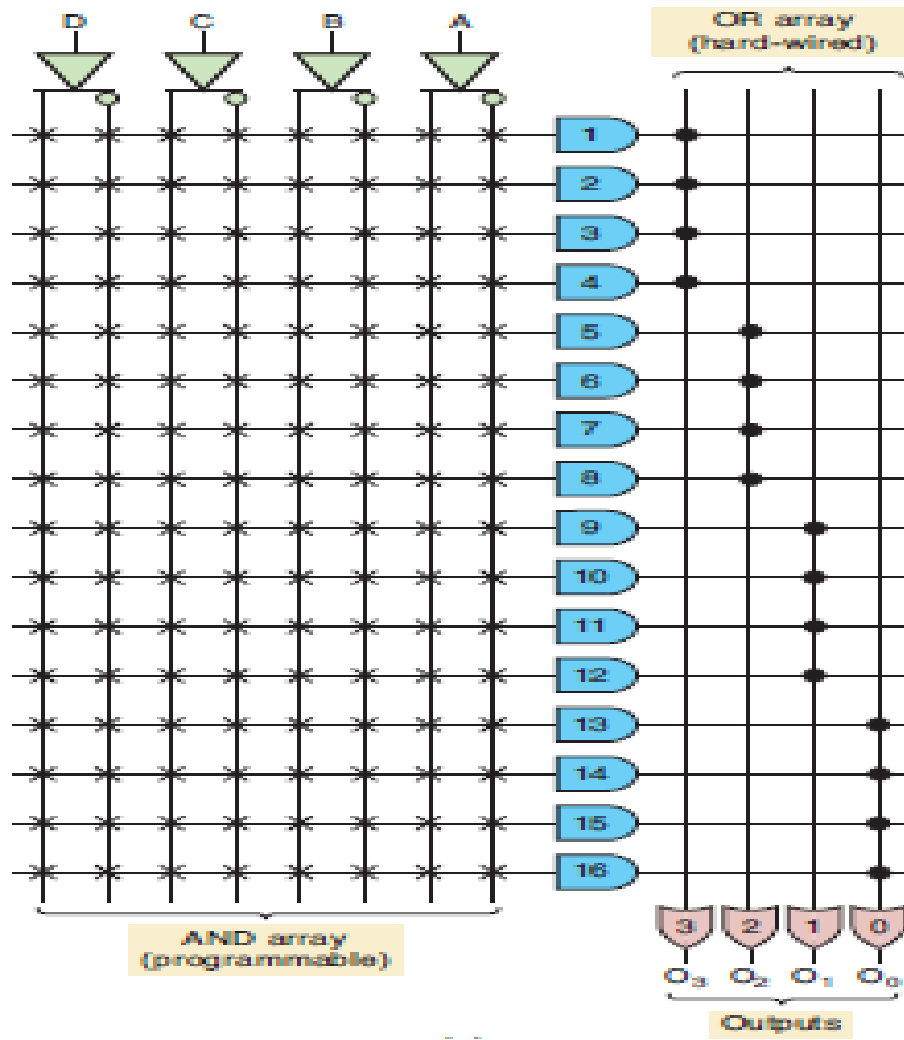


(a) Typical PAL architecture;

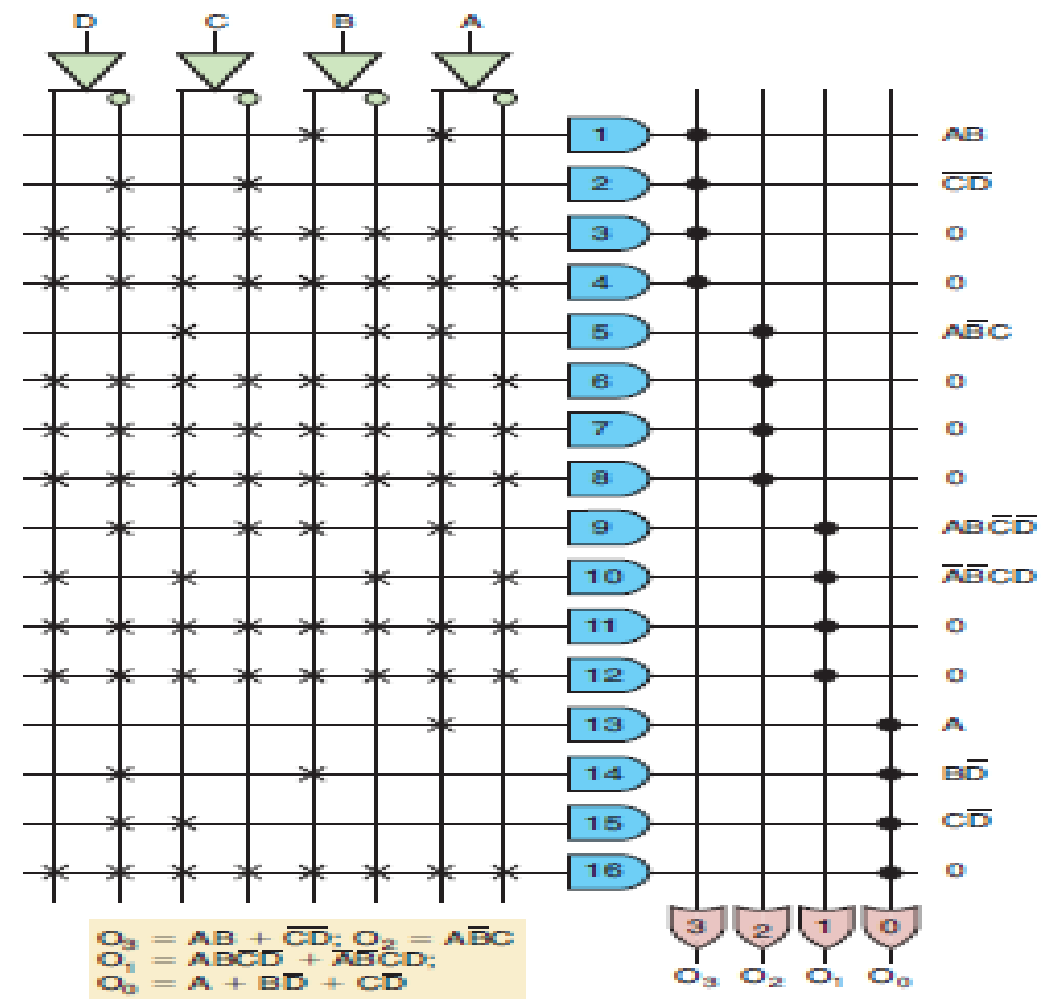


(b) the same PAL programmed for the given functions.


# PAL / GAL – General Block Diagram

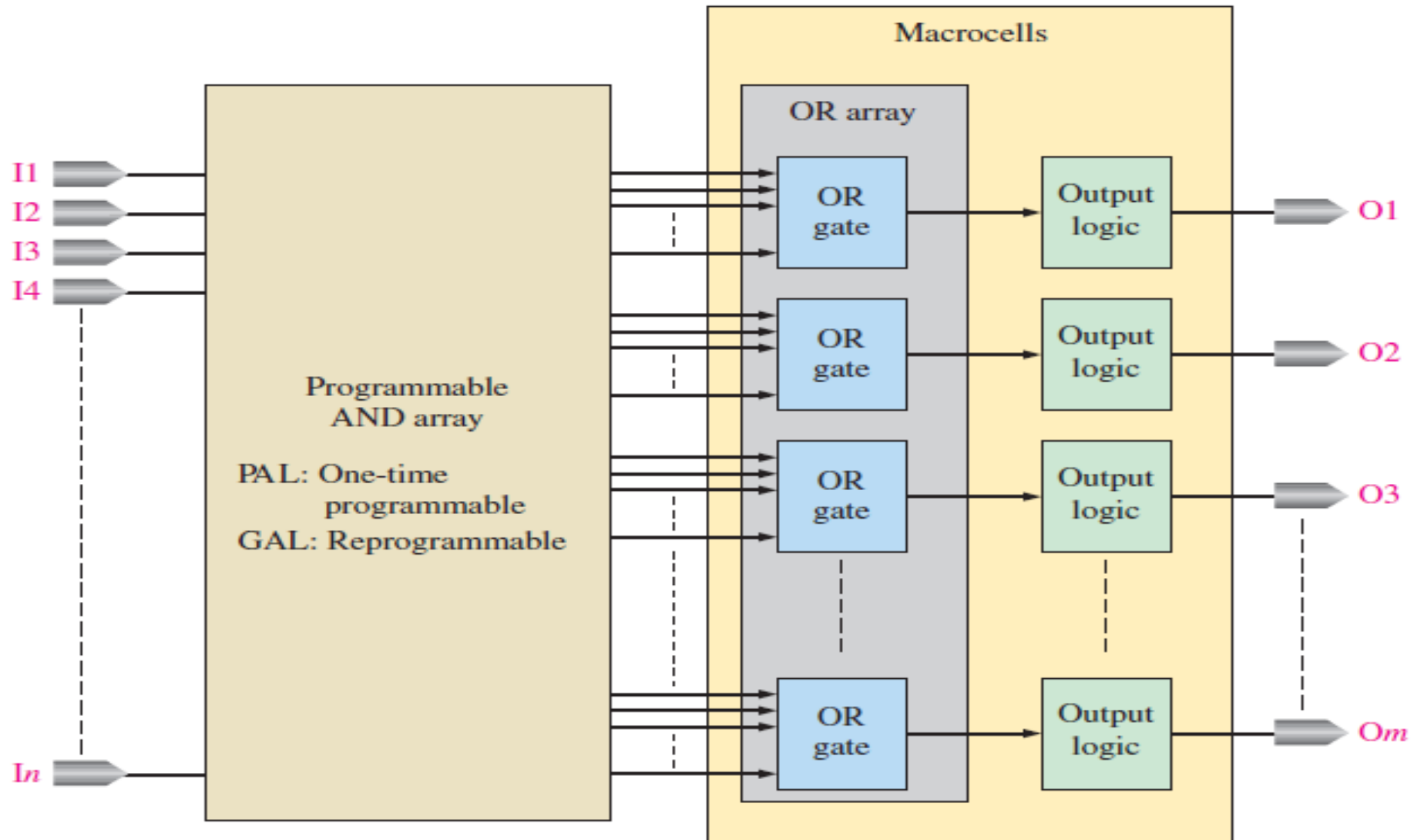


# Basic types of PAL / GAL macrocells

 

 
(a) Combinational output (active-LOW). An active-HIGH output would be shown without the bubble on the tristate gate symbol.



 (b) Combinational input/output (active-LOW)


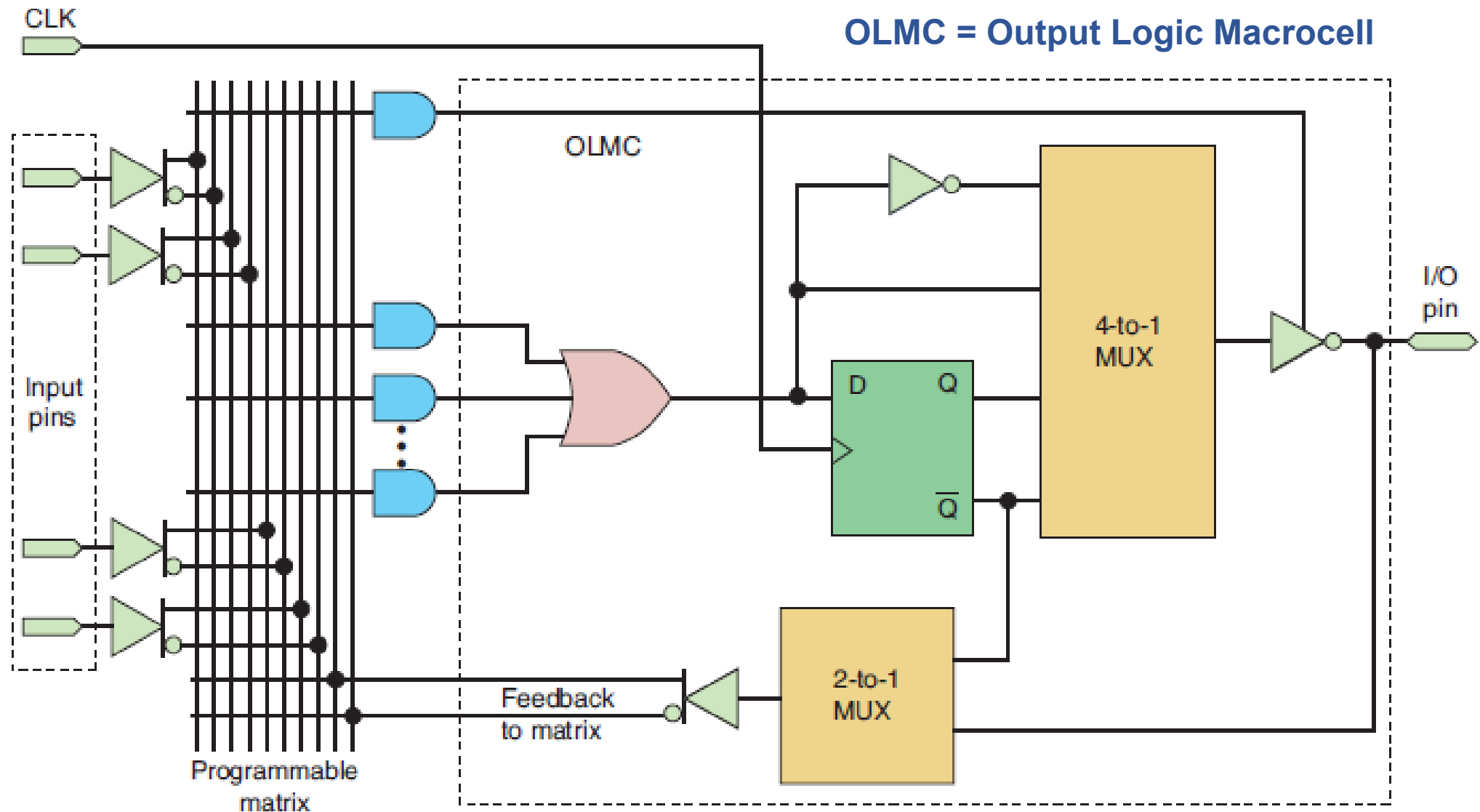
# Programmable AND matrix and OLMC in GAL devices






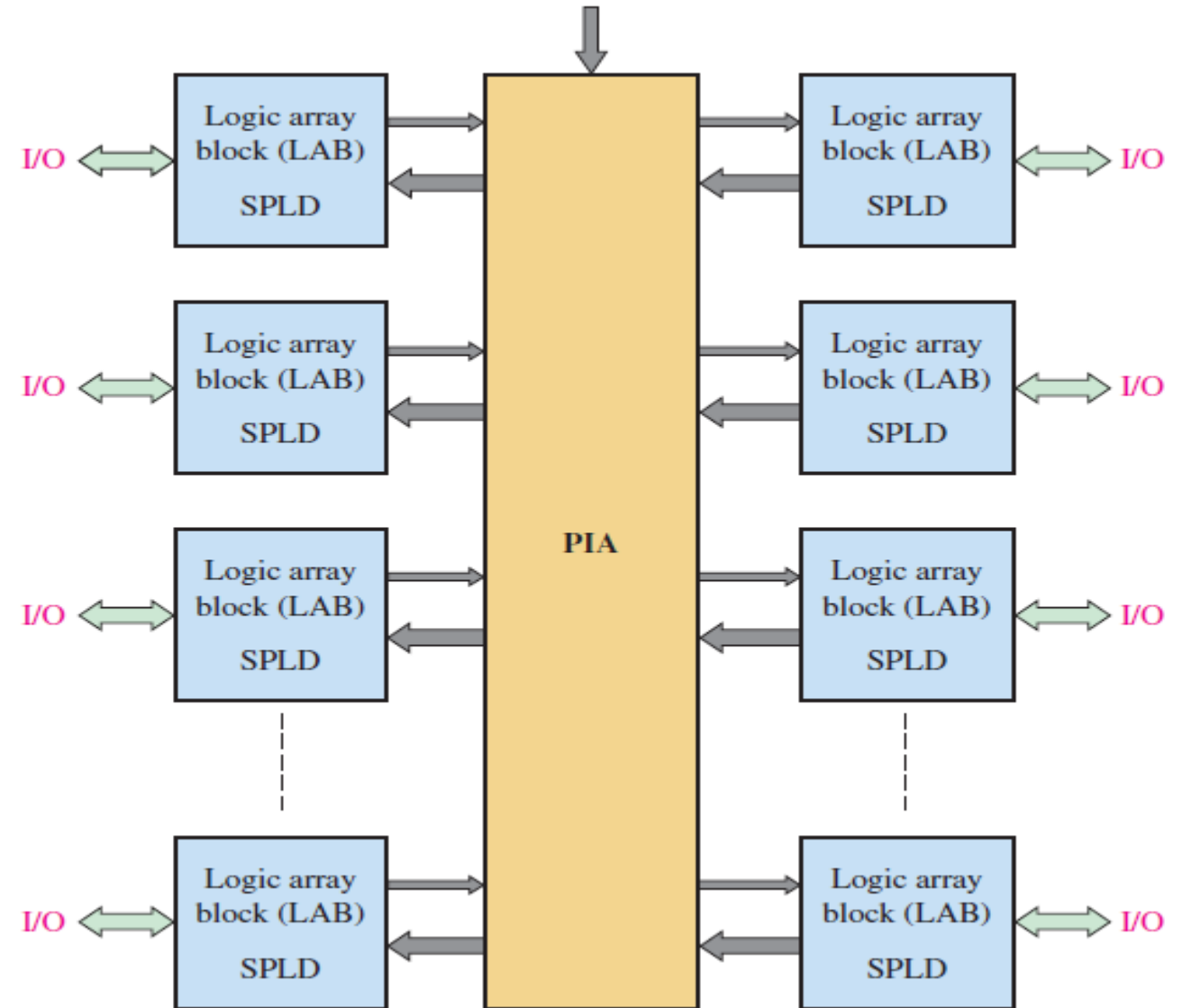
# CPLD – Complex Programmable Logic Device

- ❑ A CPLD (complex programmable logic device) consists basically of multiple SPLD arrays with programmable interconnections.


**PIA** = programmable interconnect array




# Block diagram of a typical CPLD

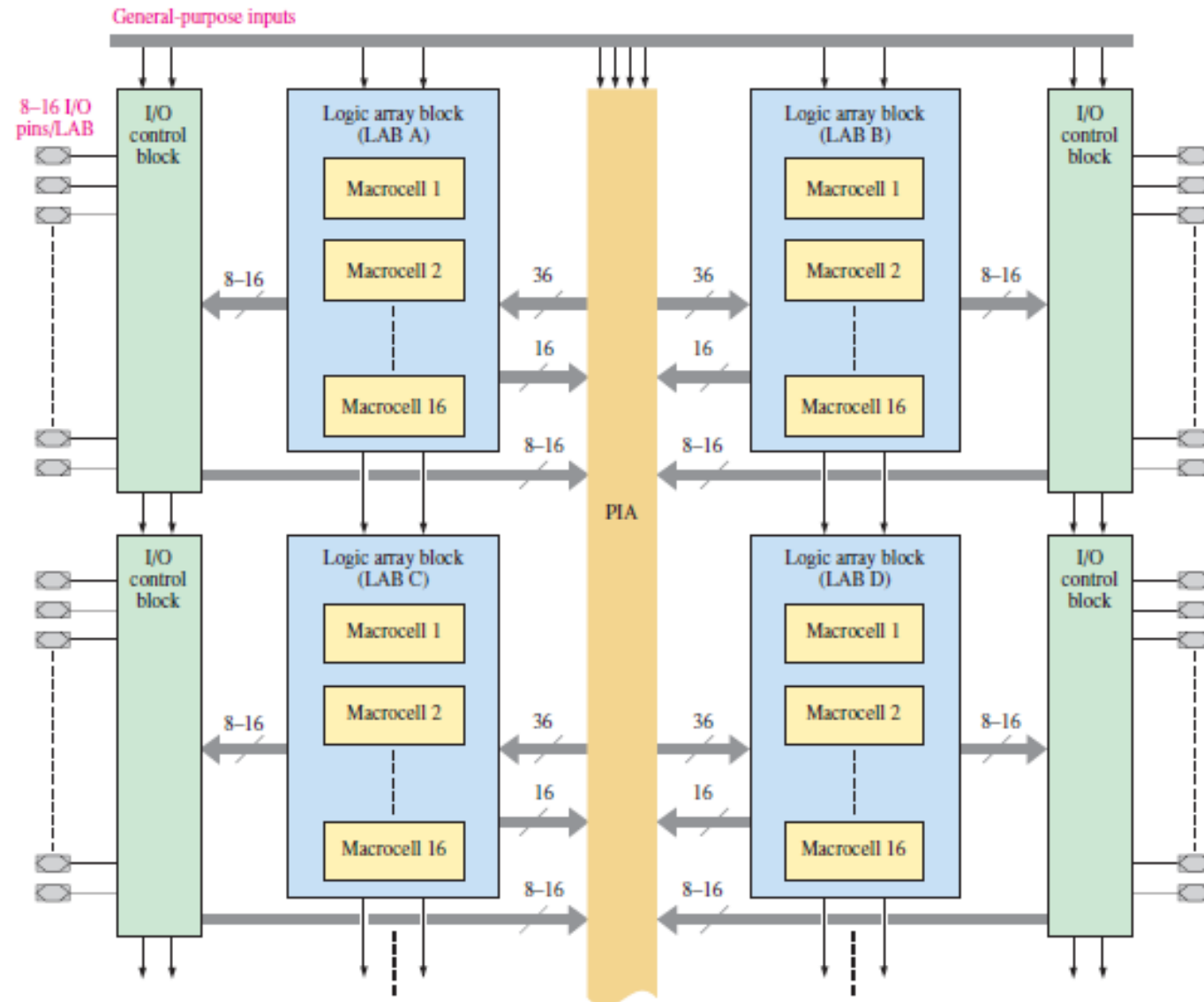

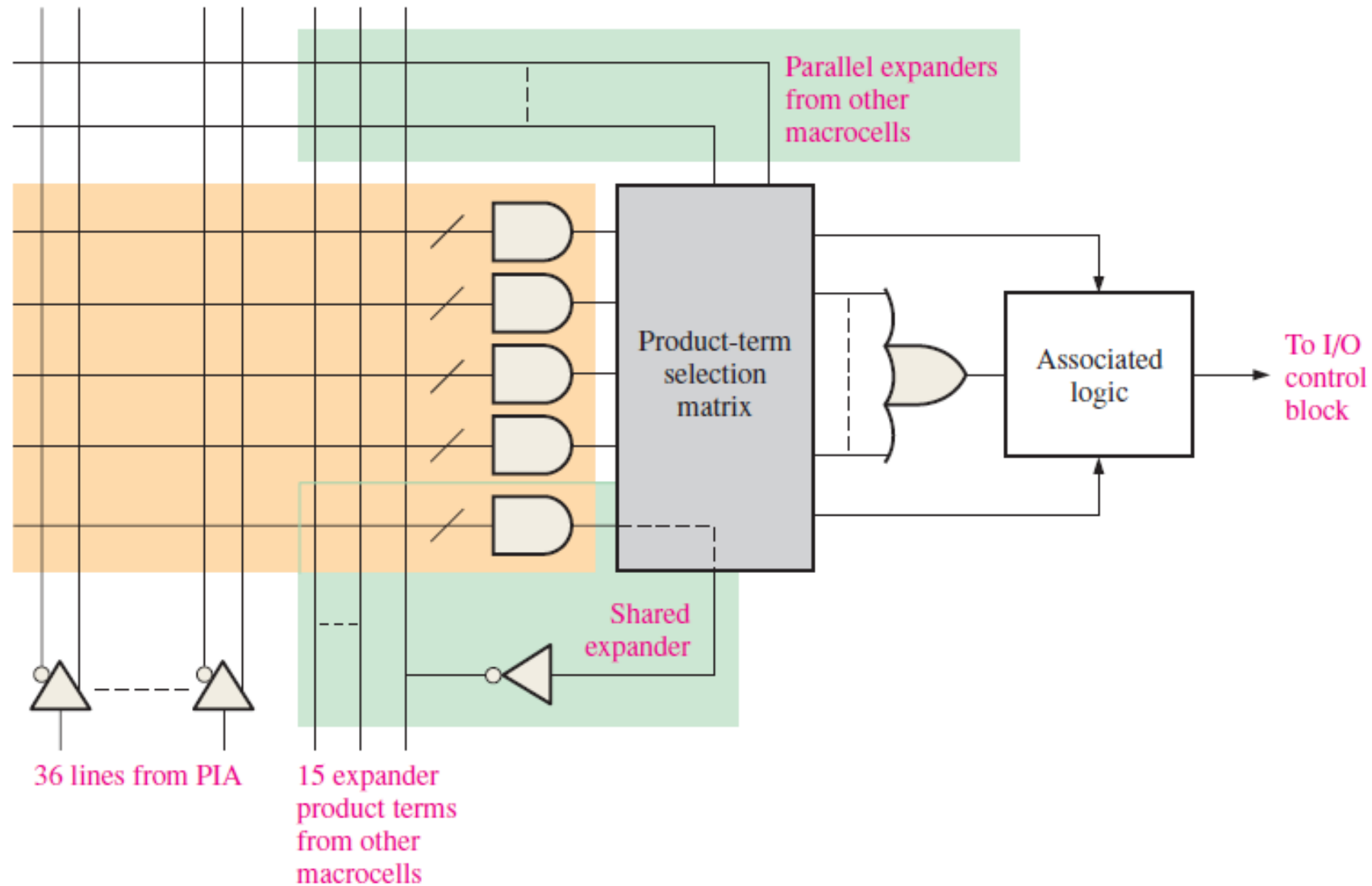
# Simplified block diagram of a typical CPLD



 

 
(a) A 4-input AND array gate can produce one 4-variable product term.





(b) AND gate is expanded to produce two product terms.

**FIGURE.** Example of how a shared expander can be used in a microcell to increase the number of product terms

**FIGURE.** Simplified illustration of using a shared expander term from another macrocell to increase an SOP expression. The red Xs and lines represent the connections produced in the hardware by the software compiler running the programmed design

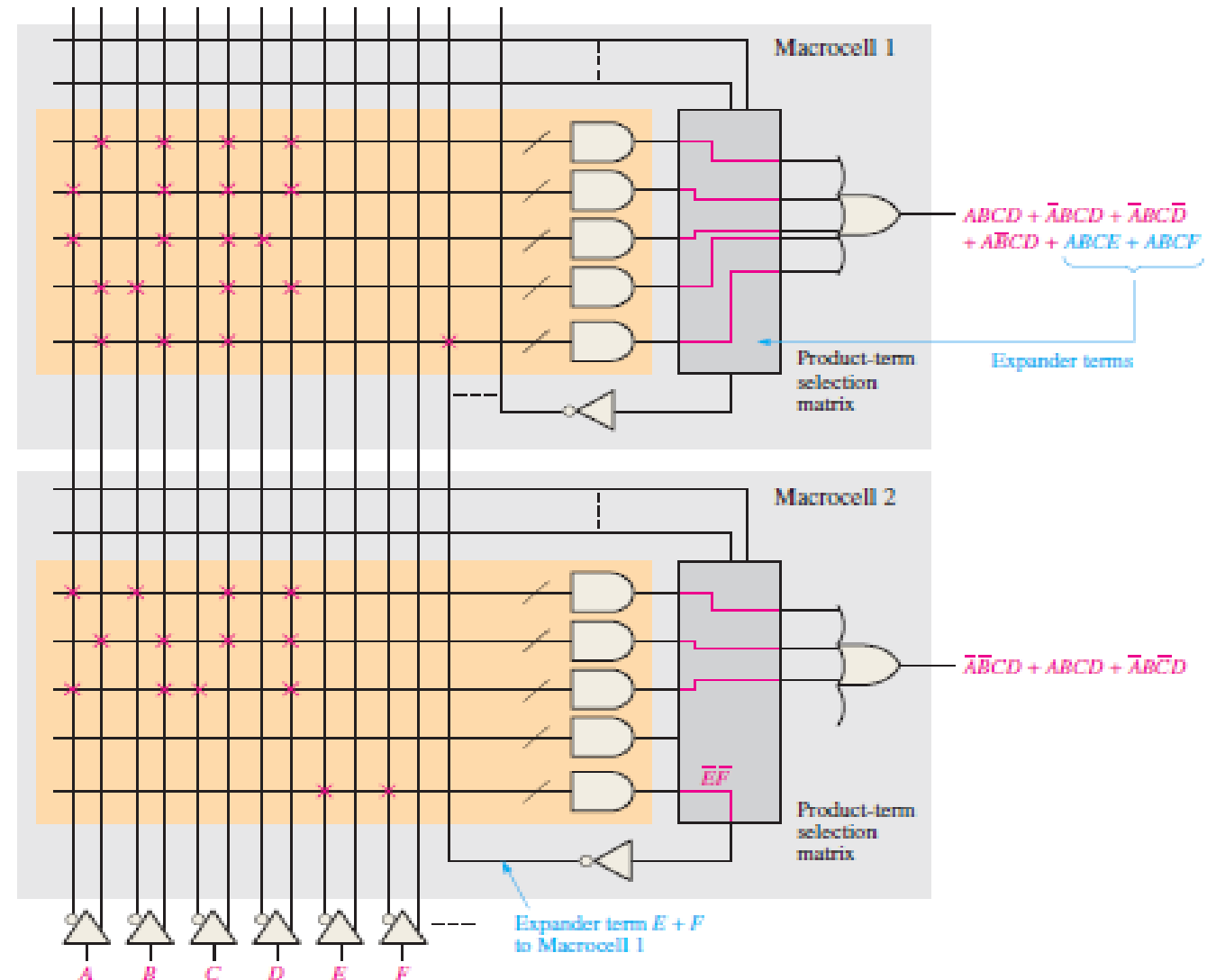

 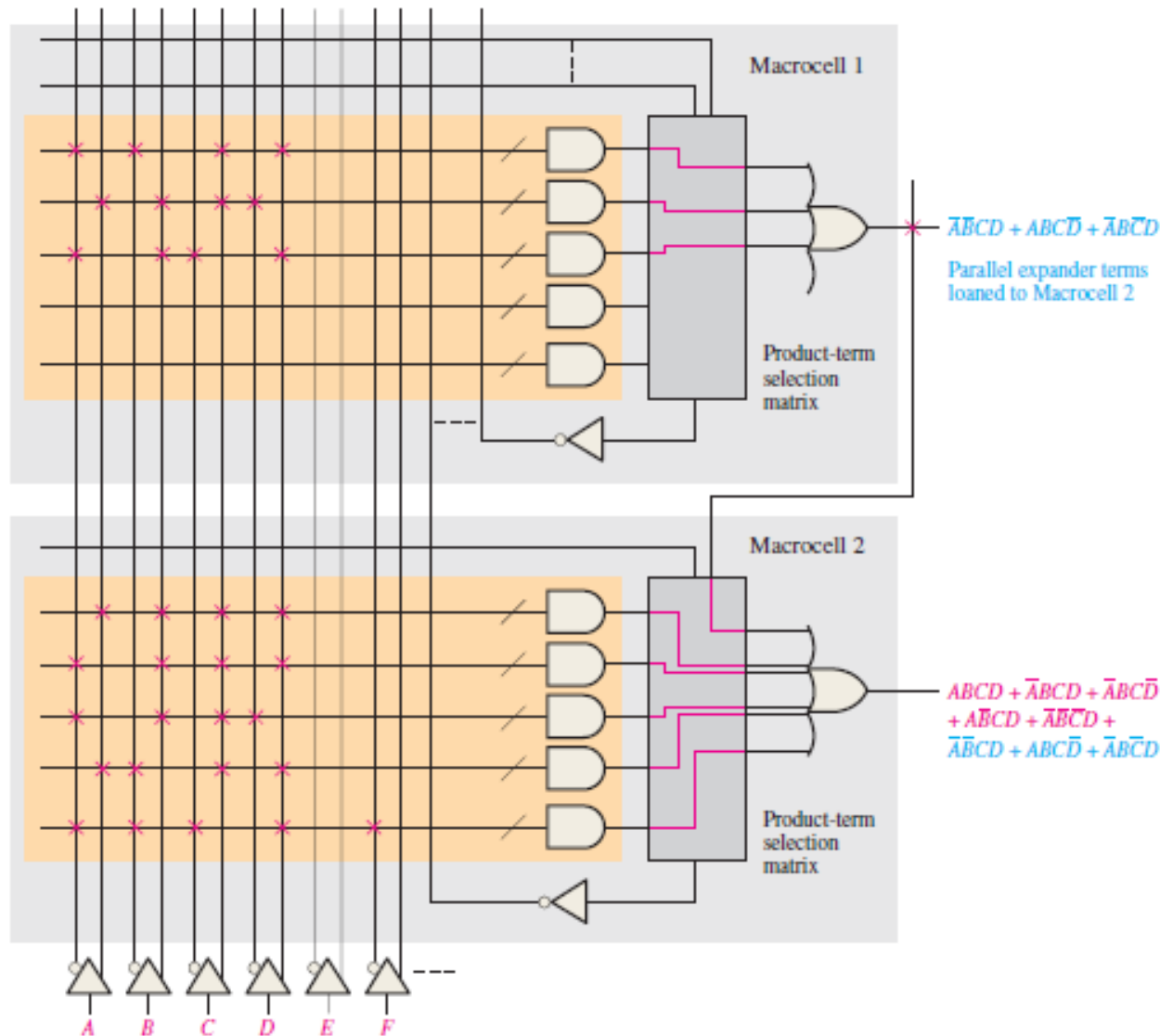
# CPLD producing SOP using parallel expander



Basic concept of the parallel expander

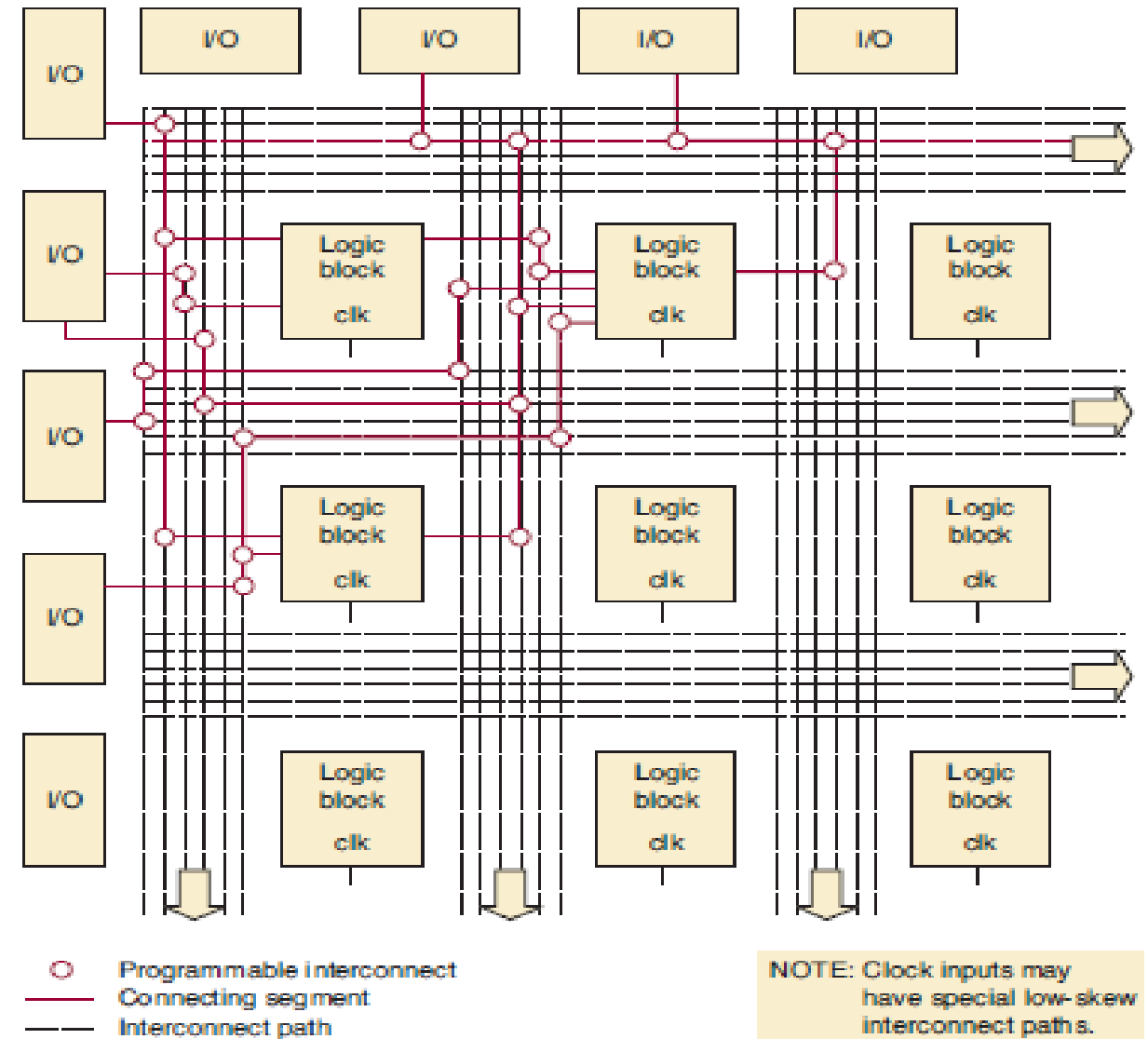
# FPGA – Field Programmable Gate Array

- ❑ An FPGA (field-programmable gate array) differs in architecture, does not use PAL/PLA type arrays, and has much greater densities than CPLDs.
- ❑ A typical FPGA has many times more equivalent gates than a typical CPLD.
- ❑ The logic-producing elements in FPGAs are generally much smaller than in CPLDs, and there are many more of them.



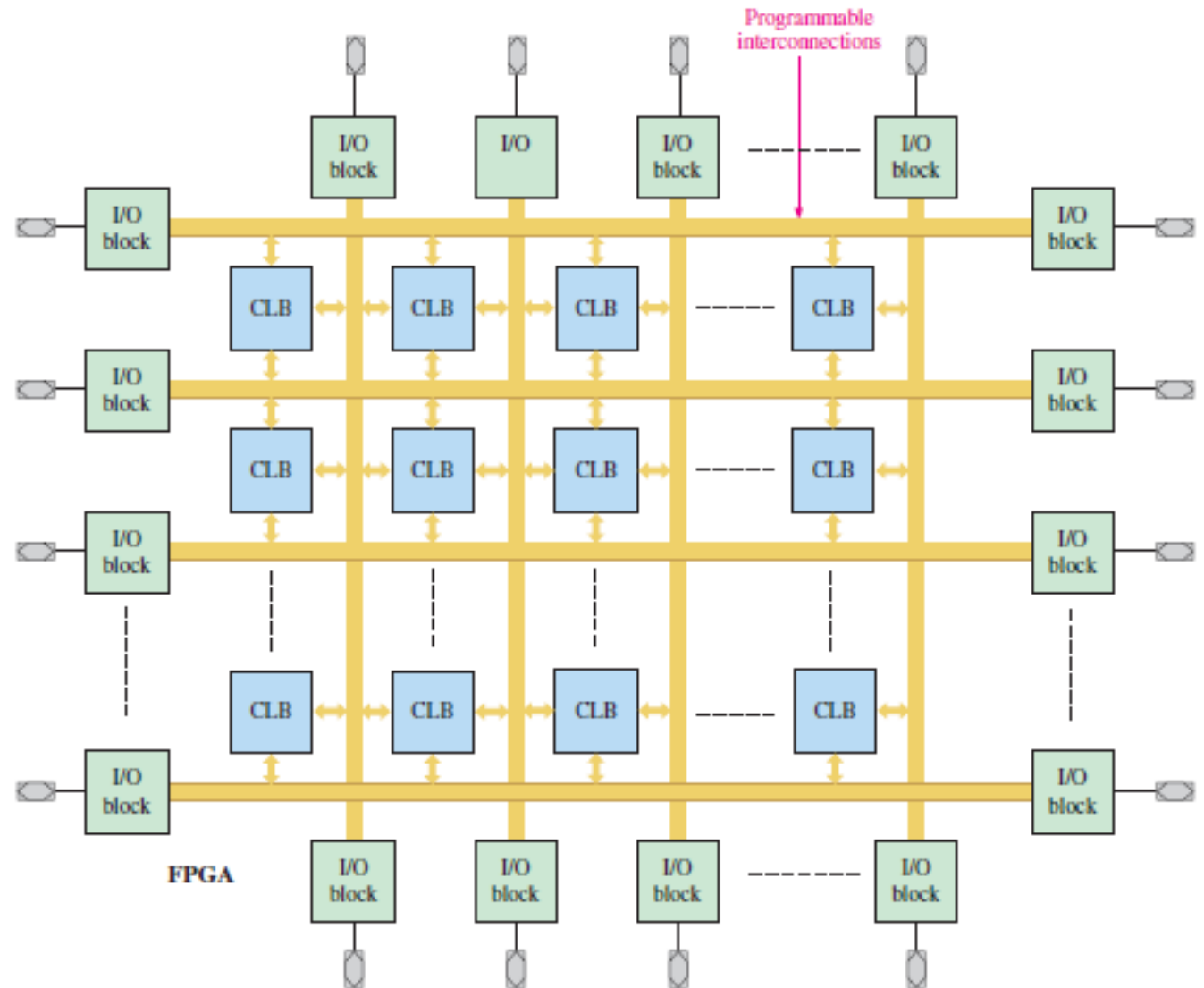
# FPGA – Field Programmable Gate Array

- ❑ The three basic elements in an FPGA are
  - ✓ the configurable logic block (CLB),
  - ✓ the interconnections, and
  - ✓ the input/output (I/O) blocks






# Basic configurable logic blocks (CLBs)

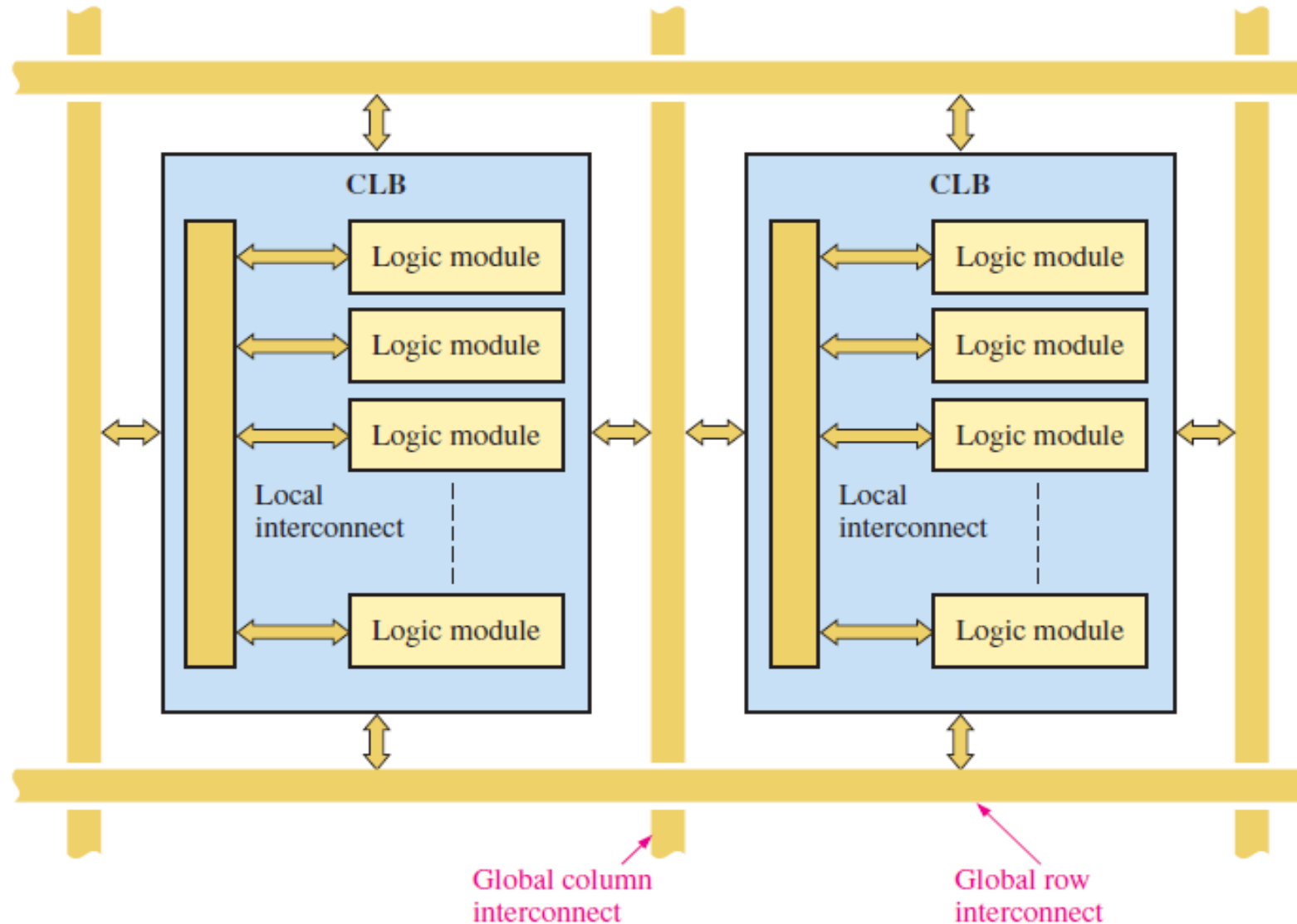

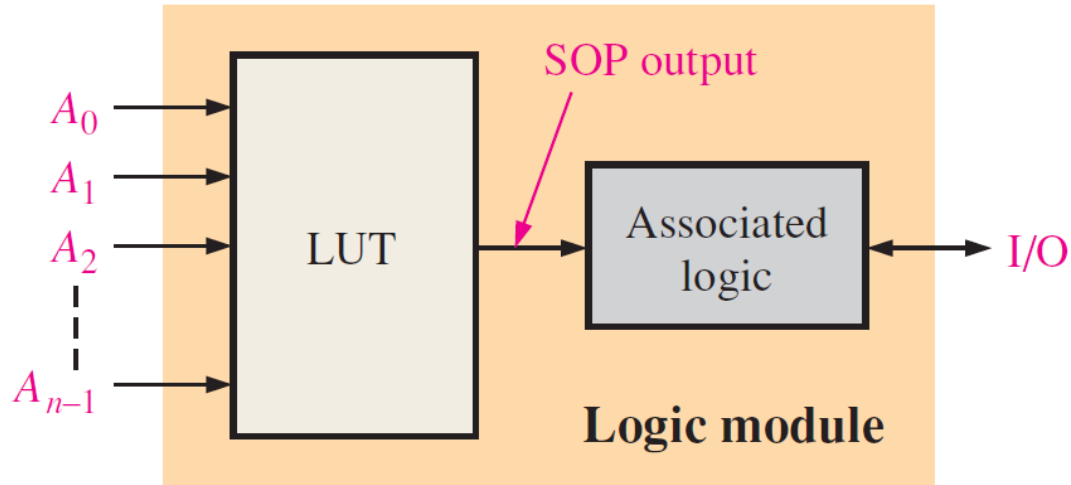
# FPGA logic module and look-up table (LUT)




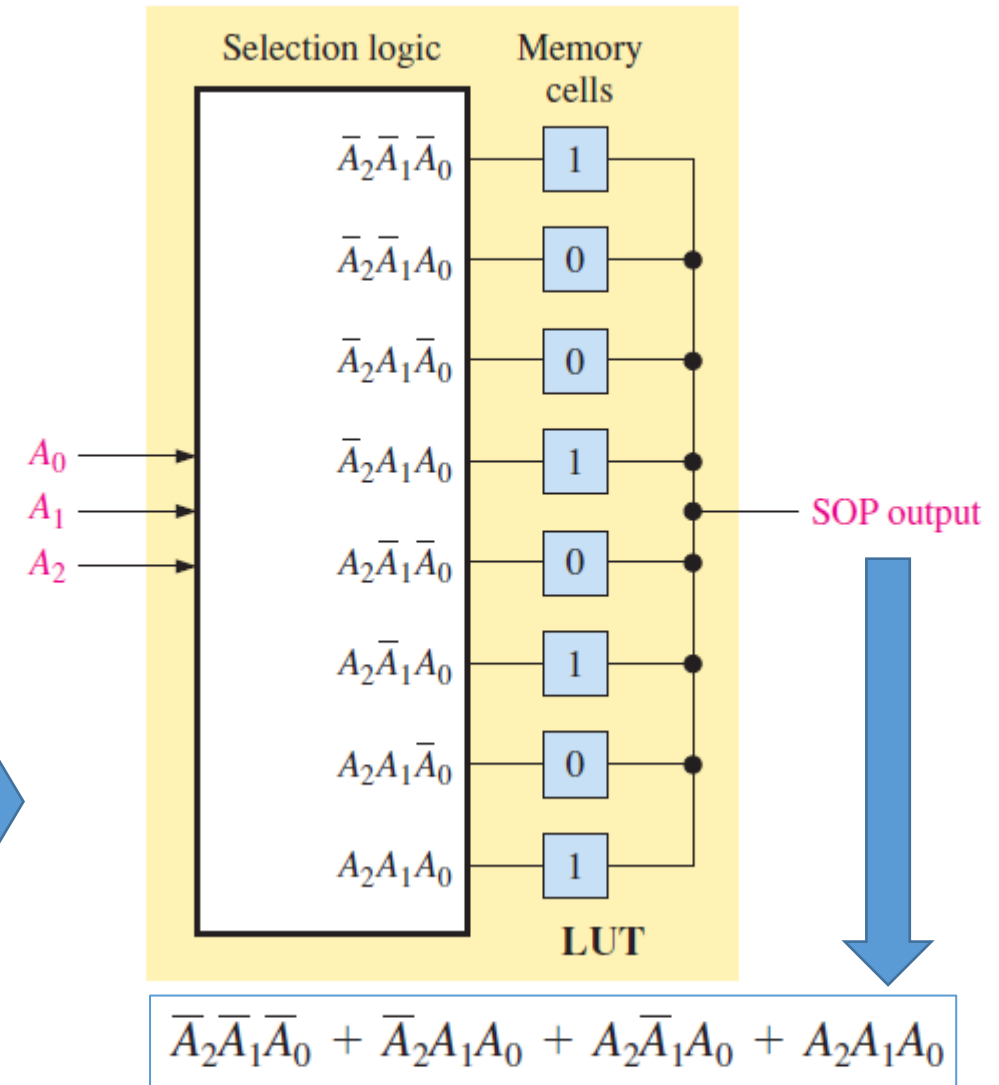**FPGA logic module**

number of memory cells equal to  $2^n$ , where  $n$  is the number of input variables




# Possible look-up table (LUT) configuration in a logic module

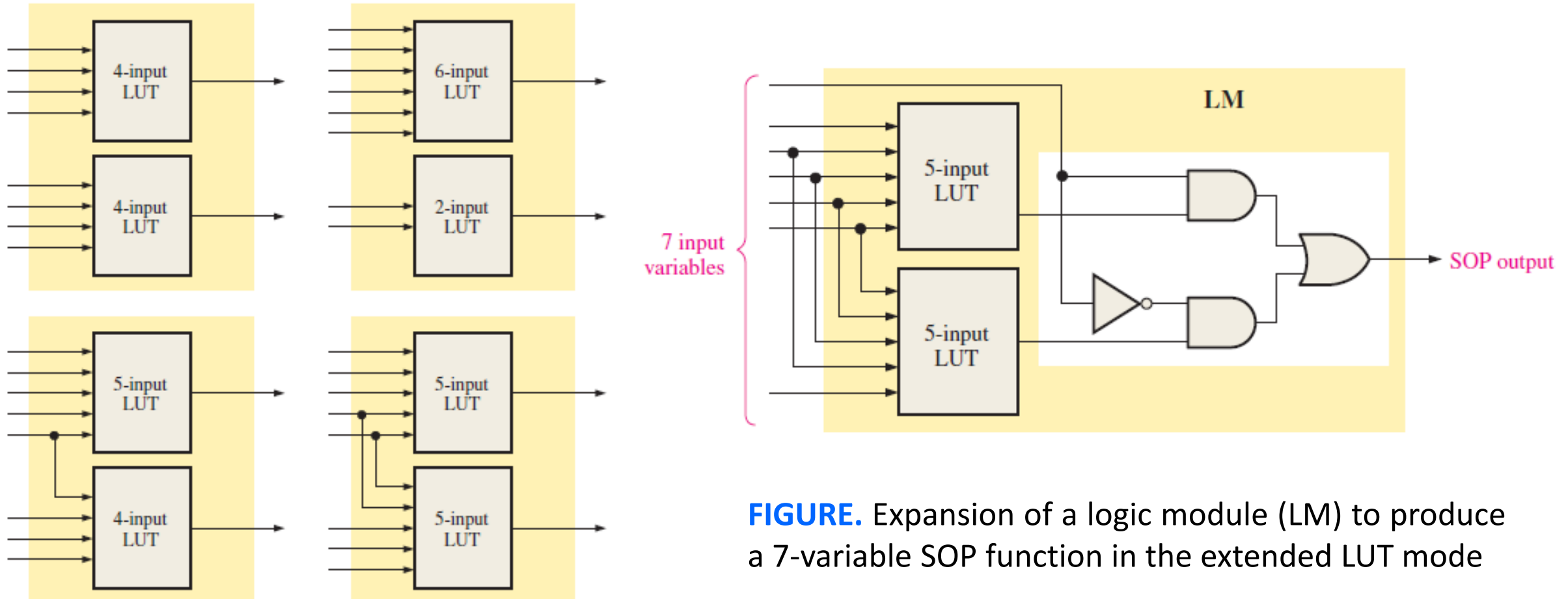

**FIGURE.** Expansion of a logic module (LM) to produce a 7-variable SOP function in the extended LUT mode

# Example

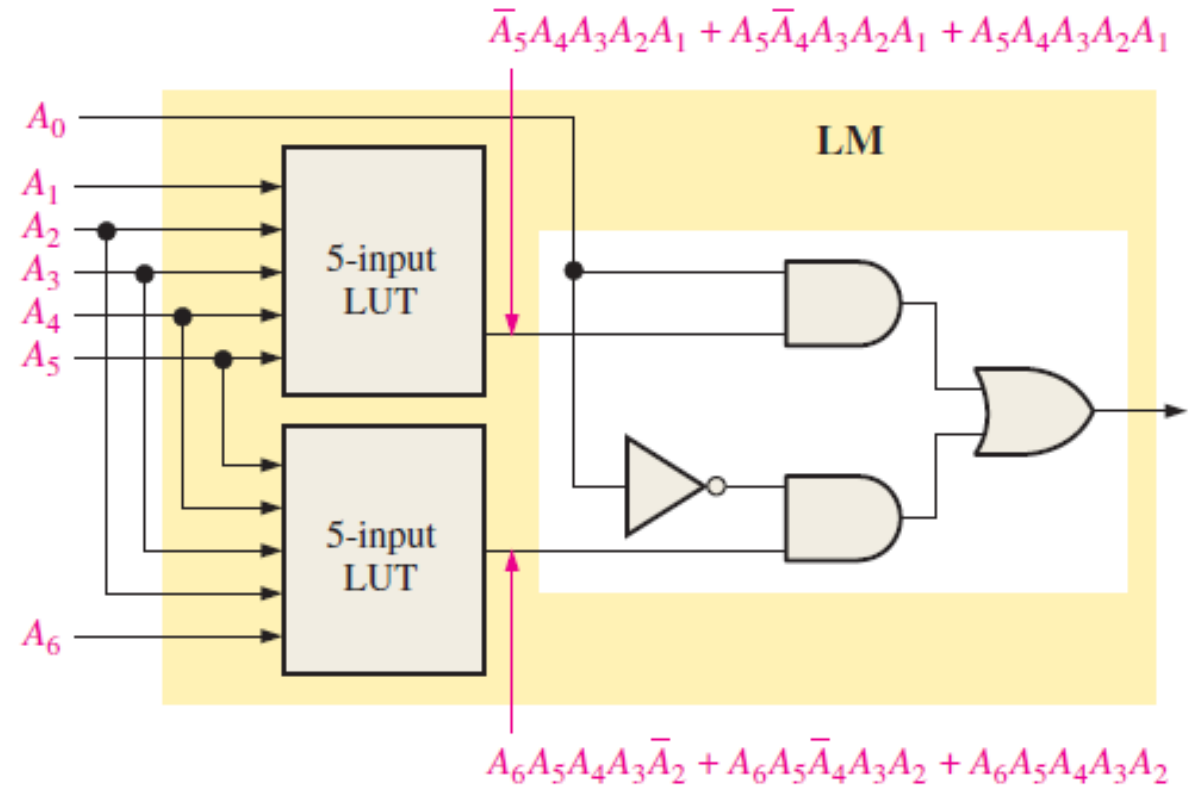**PROBLEM.** A logic module is configured in the extended LUT mode, as shown in Figure 10–30. For the specific LUT outputs shown, determine the final SOP output



## Solution

The SOP output expression is as follows:

$$\bar{A}_5A_4A_3A_2A_1A_0 + A_5\bar{A}_4A_3A_2A_1A_0 + A_5A_4A_3A_2A_1A_0 + A_6A_5A_4A_3\bar{A}_2\bar{A}_0 + A_6A_5\bar{A}_4A_3A_2\bar{A}_0 + A_6A_5A_4A_3A_2\bar{A}_0$$



# References

1. ***Digital Fundamentals*** by Thomas Floyd, Pearson International Edition, 11<sup>th</sup> Edition, Chapter 9, Page 561-627.
2. ***Digital Systems: Principles and Applications*** by Ronald Tocci, Neal Widmer and Greg Moss, Pearson International Edition, 12th Edition, Chapter 7, Page 941-961.



# Next ?



**Final Exam**