



Lecture – 7

Shift Registers

Lesson Outcomes

After completing this lecture, students will be able to

- *Identify the basic forms of data movement in shift registers*
- *Explain how serial in/serial out, serial in/parallel out, parallel in/serial out, and parallel in/parallel out shift registers operate*
- *Describe how a bidirectional shift register*
- *Use a shift register as a counter*
- *Use a shift register as a time-delay device*



Key Terms

BIDIRECTIONAL Having two directions. In a bidirectional shift register, the stored data can be shifted right or left.

LOAD To enter data into a shift register.

REGISTER One or more flip-flops used to store and shift data.

STAGE One storage element in a register.



Register

- ❑ A *register* is a digital circuit with two basic functions: *data storage* and *data movement*. The storage capability of a register makes it an important type of *memory device*.
- ❑ The *storage capacity* of a register is the total number of bits (1s and 0s) of digital data it can retain. Each stage (flip-flop) in a shift register represents one bit of storage capacity; therefore, the number of stages in a register determines its storage capacity.
- ❑ The *shift capability* of a register permits the movement of data from stage to stage within the register or into or out of the register upon application of clock pulses.
- ❑ There are four types of shift registers based on data input and output (inputs/outputs): *serial in/serial out*, *serial in/parallel out*, *parallel in/serial out*, and *parallel in/parallel out*.

Shift Register Operation

- When 1 is applied to the data input as shown, and a clock pulse is applied that stores the 1 by setting the flip-flop. When the 1 on the input is removed, the flip-flop remains in the SET state, thereby storing the 1. A similar procedure applies to the storage of a 0 by resetting the flip-flop.

 
 


FIGURE 8-1 The flip-flop as a storage element.

Data movement in shift register

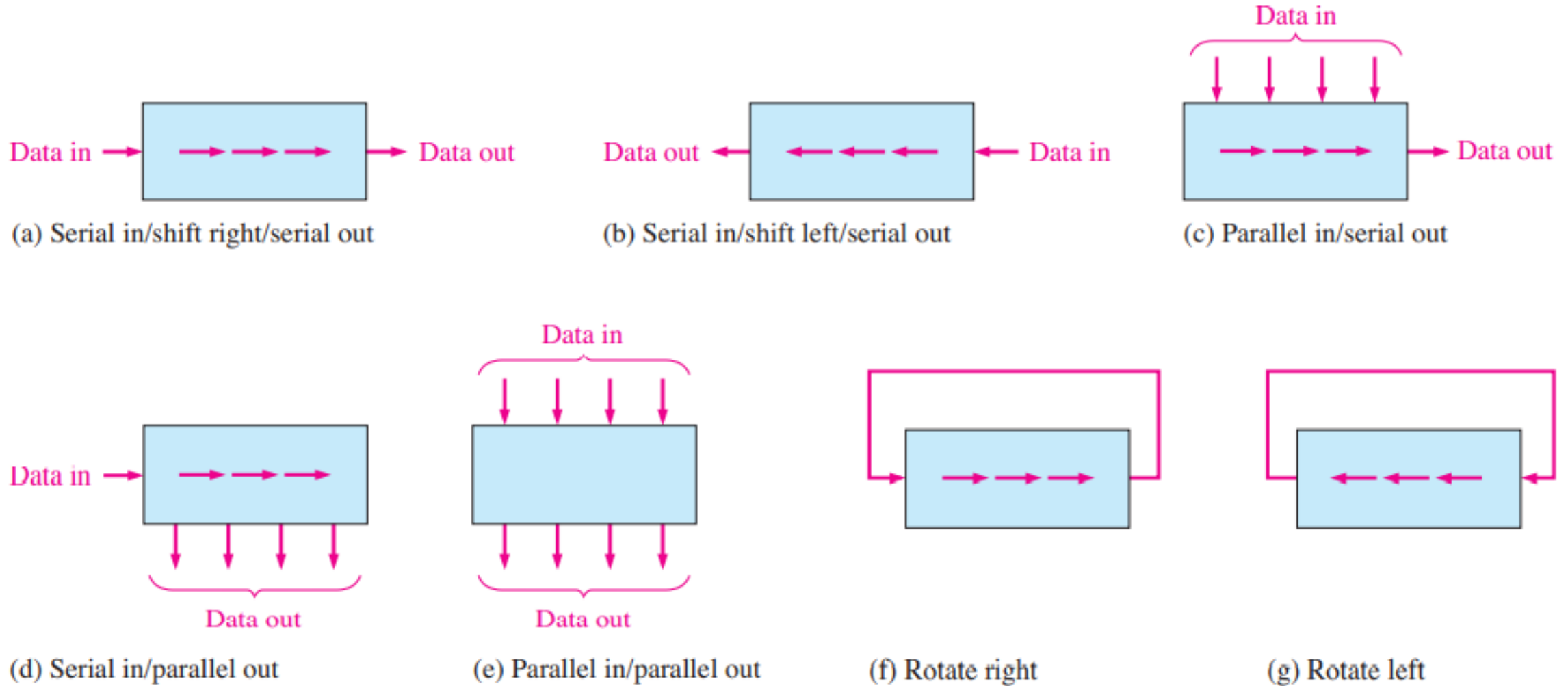


FIGURE 8-2 Basic data movement in shift registers. (Four bits are used for illustration. The bits move in the direction of the arrows.)

Serial in / Serial out shift register

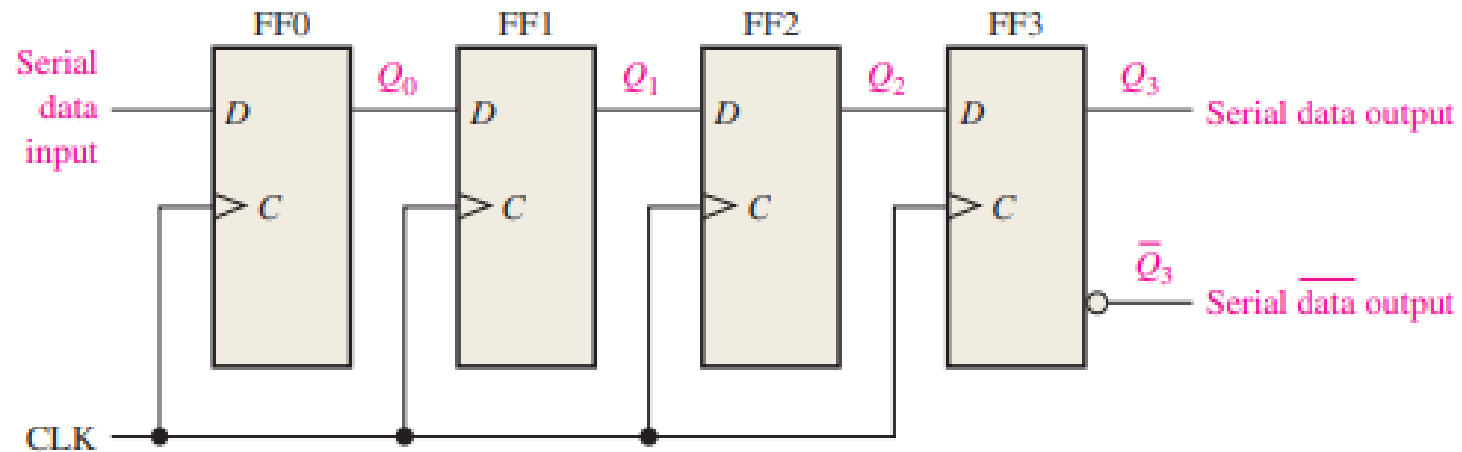


FIGURE 8–3 Serial in/serial out shift register.

TABLE 8–1

Shifting a 4-bit code into the shift register in Figure 8–3. Data bits are indicated by a beige screen.

CLK	FF0 (Q_0)	FF1 (Q_1)	FF2 (Q_2)	FF3 (Q_3)
Initial	0	0	0	0
1	0	0	0	0
2	1	0	0	0
3	0	1	0	0
4	1	0	1	0



TABLE 8–2

Shifting a 4-bit code out of the shift register in Figure 8–3. Data bits are indicated by a beige screen.



CLK	FF0 (Q_0)	FF1 (Q_1)	FF2 (Q_2)	FF3 (Q_3)
Initial	1	0	1	0
5	0	1	0	1
6	0	0	1	0
7	0	0	0	1
8	0	0	0	0

Example

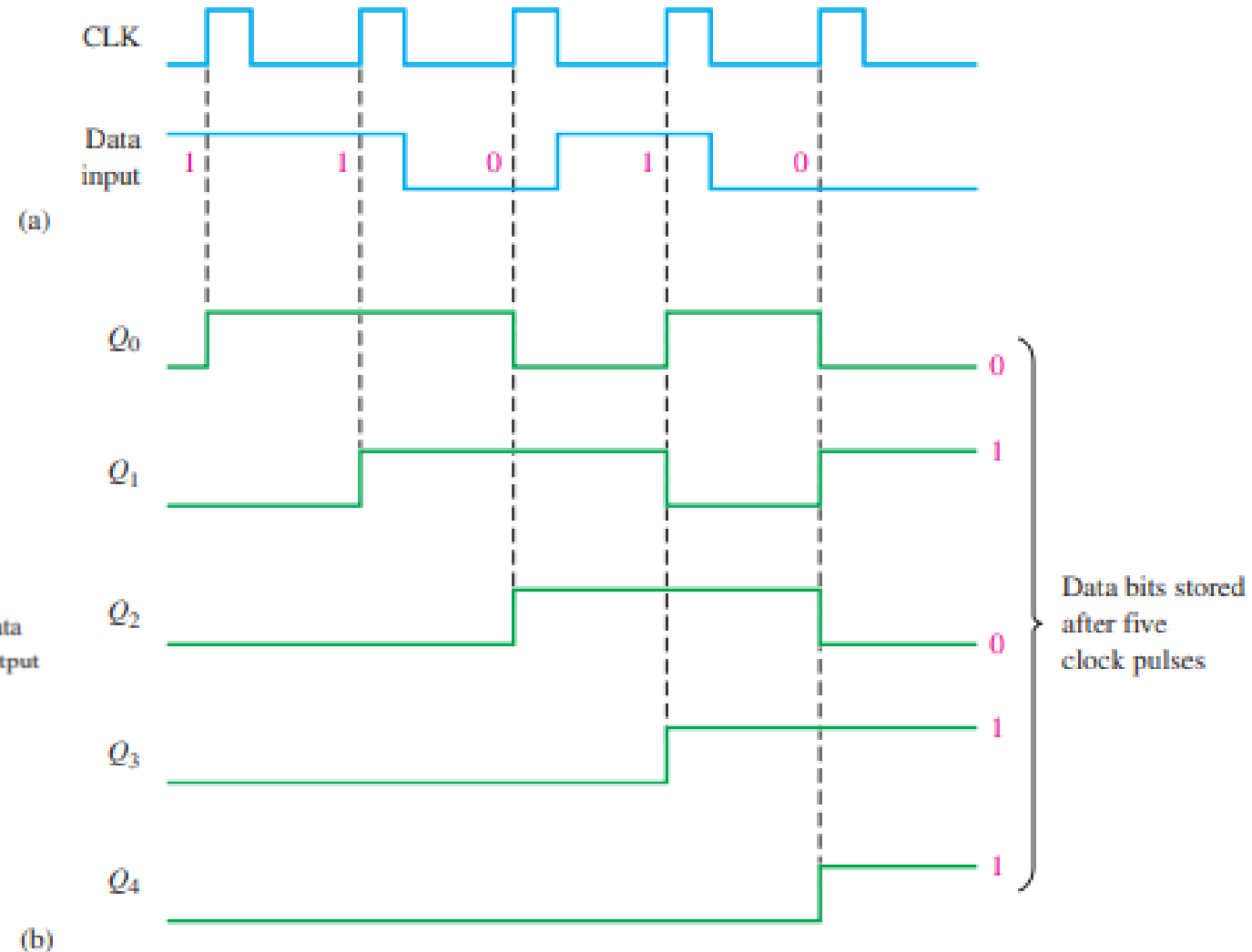
 
PROBLEM. Show the states of the 5-bit register in Figure (a) for the specified data input and clock waveforms. Assume that the register is initially cleared (all 0s).





Serial in parallel out register

  

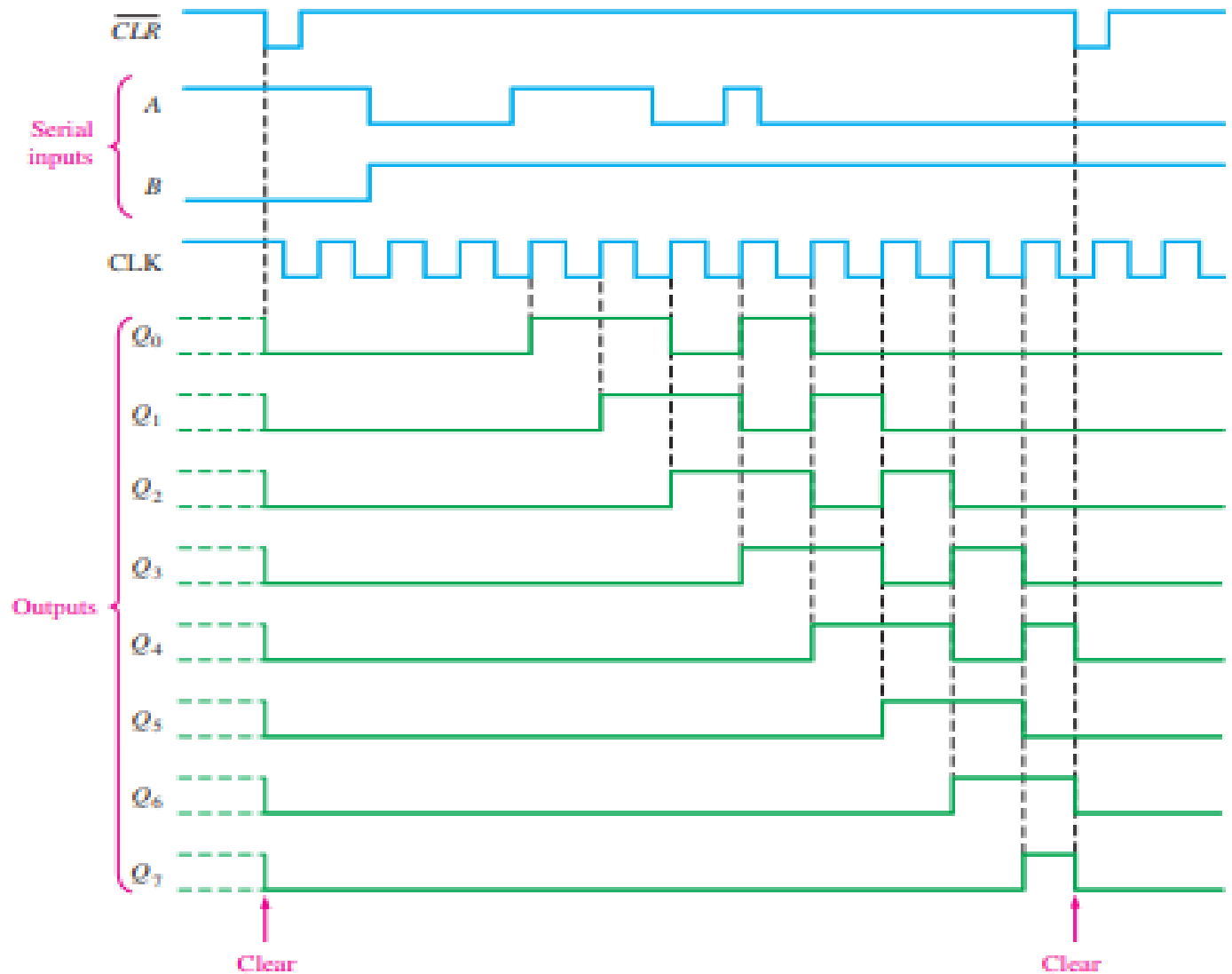 74HC164 8-bit serial in/parallel out shift register




Parallel in serial out register

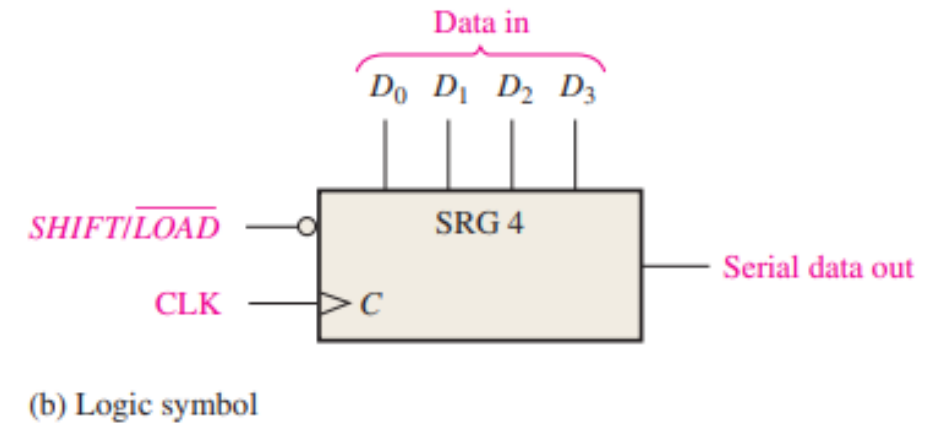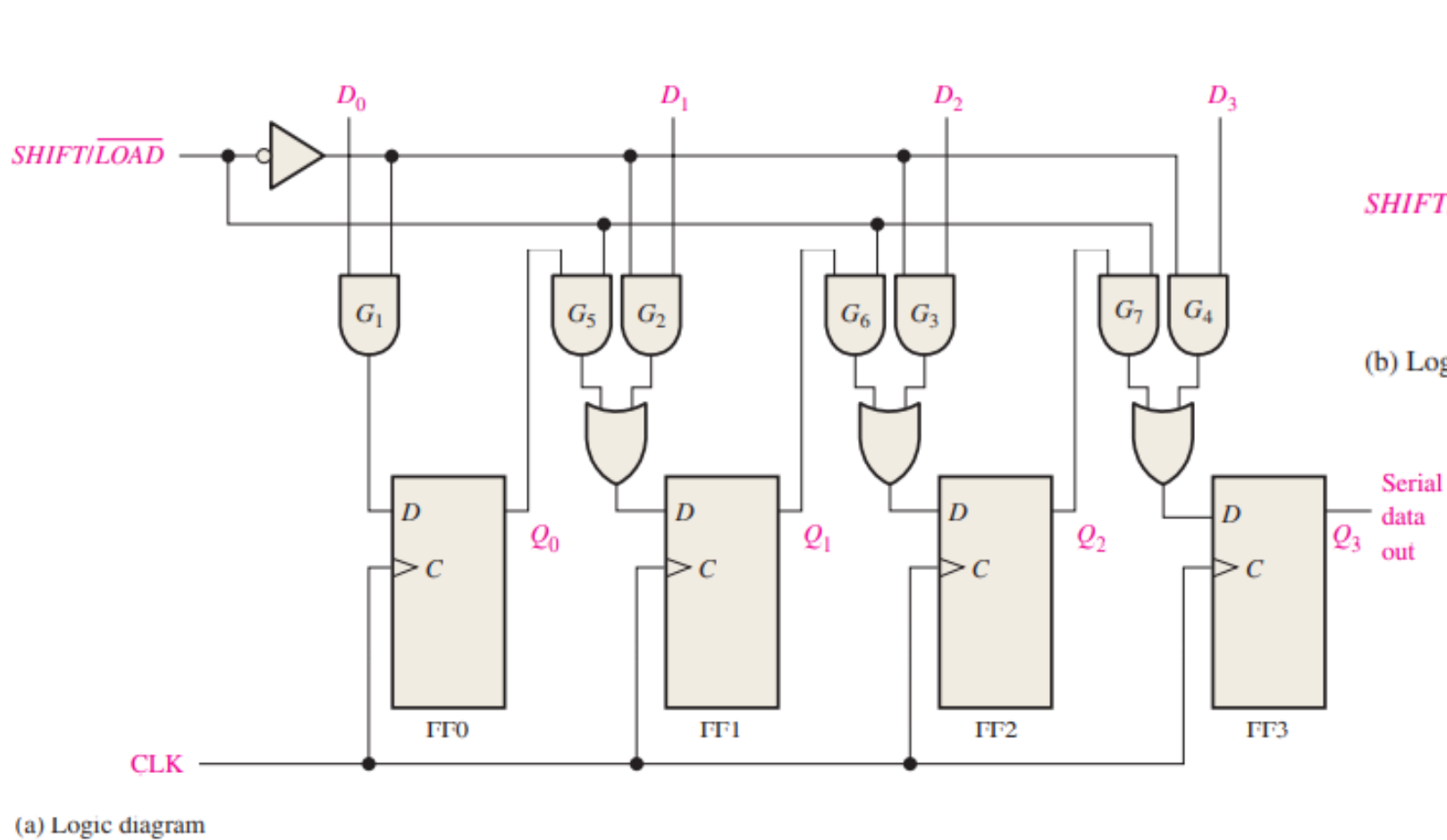

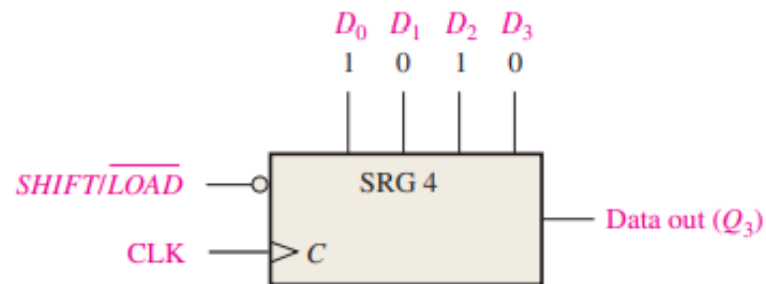
EXAMPLE 8-3

Show the data-output waveform for a 4-bit register with the parallel input data and the clock and *SHIFT/LOAD* waveforms given in Figure 8-11(a). Refer to Figure 8-10(a) for the logic diagram.





Solution



On clock pulse 1, the parallel data ($D_0D_1D_2D_3 = 1010$) are loaded into the register, making Q_3 a 0. On clock pulse 2 the 1 from Q_2 is shifted onto Q_3 ; on clock pulse 3 the 0 is shifted onto Q_3 ; on clock pulse 4 the last data bit (1) is shifted onto Q_3 ; and on clock pulse 5, all data bits have been shifted out, and only 1s remain in the register (assuming the D_0 input remains a 1). See Figure 8-11(b).

 

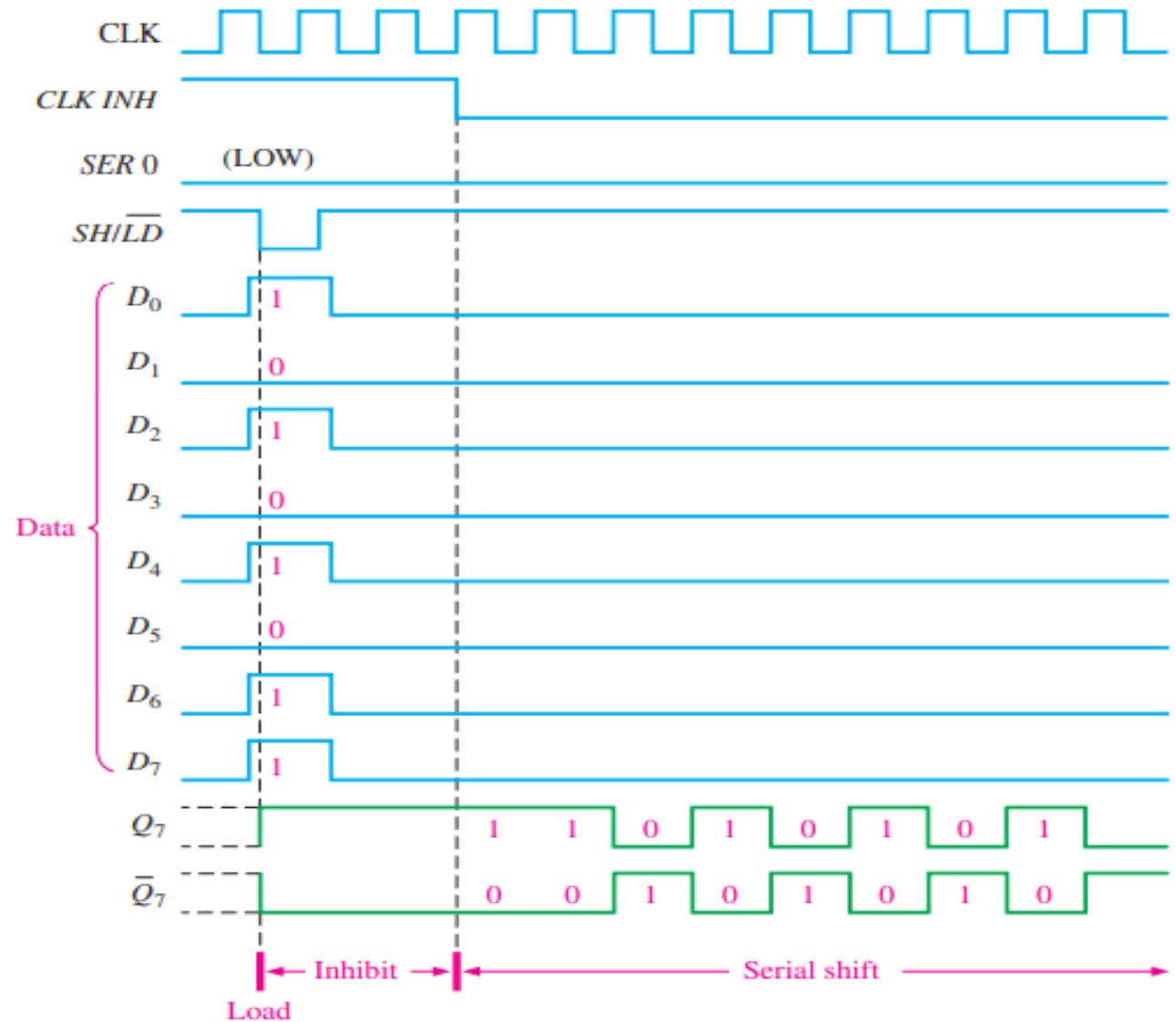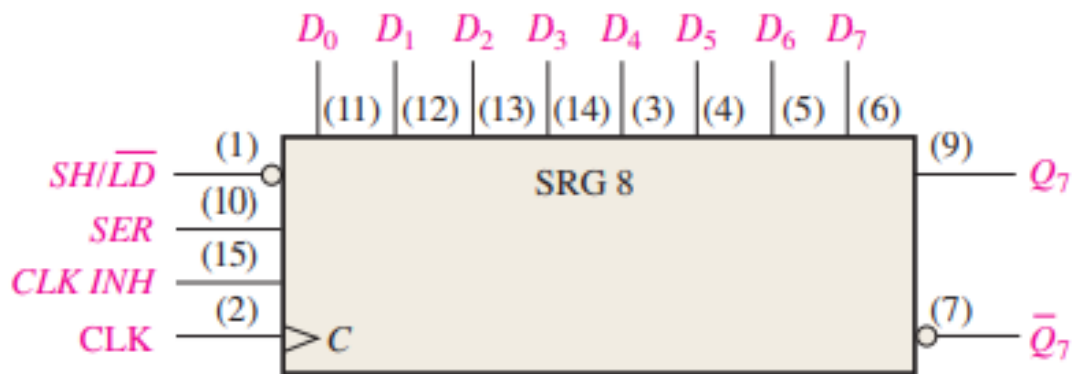74HC165 8-bit parallel load shift register





Parallel in parallel out register

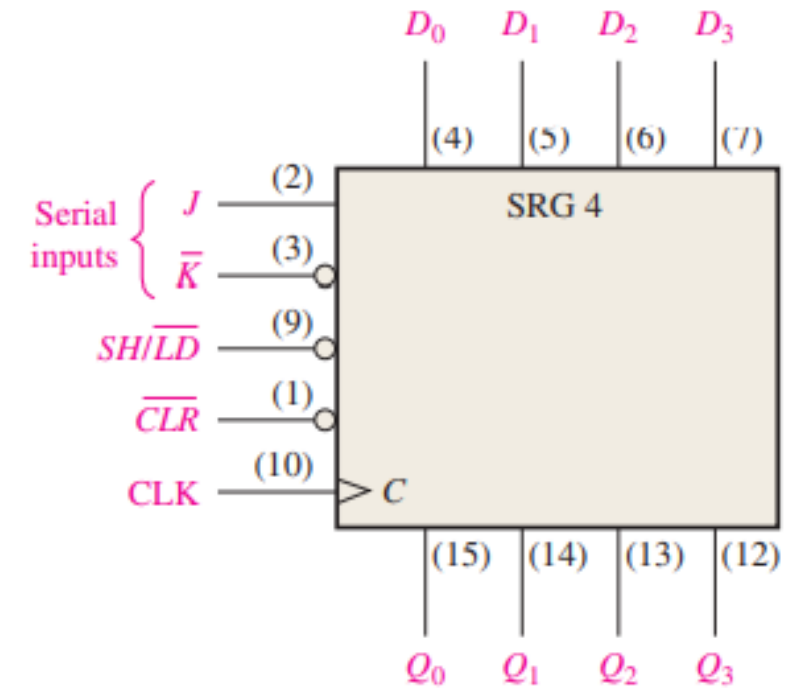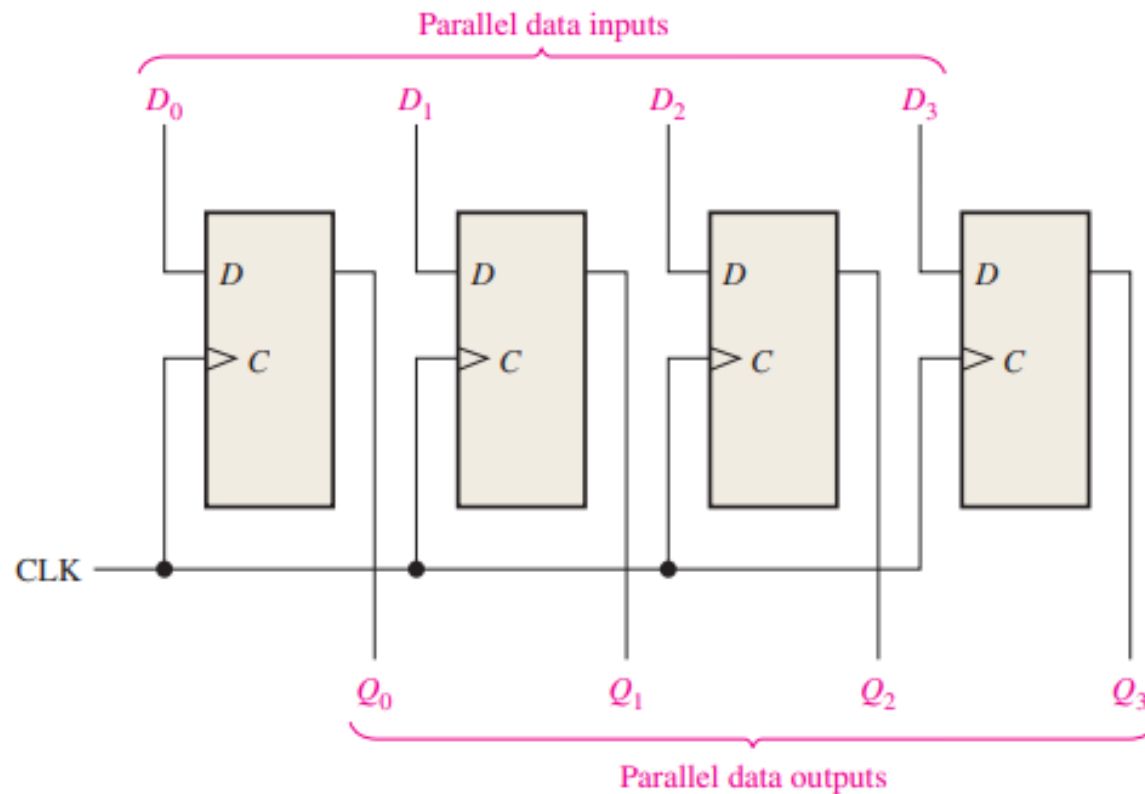

The 74HC195 4-bit parallel access shift register.


When the $SHIFT/LOAD$ input (SH/\overline{LD}) is LOW, the data on the parallel inputs are entered synchronously on the positive transition of the clock. When (SH/\overline{LD}) is HIGH, stored data will shift right (Q_0 to Q_3) synchronously with the clock. Inputs J and \overline{K} are the serial data inputs to the first stage of the register (Q_0); Q_3 can be used for serial output data. The active-LOW clear input is asynchronous.

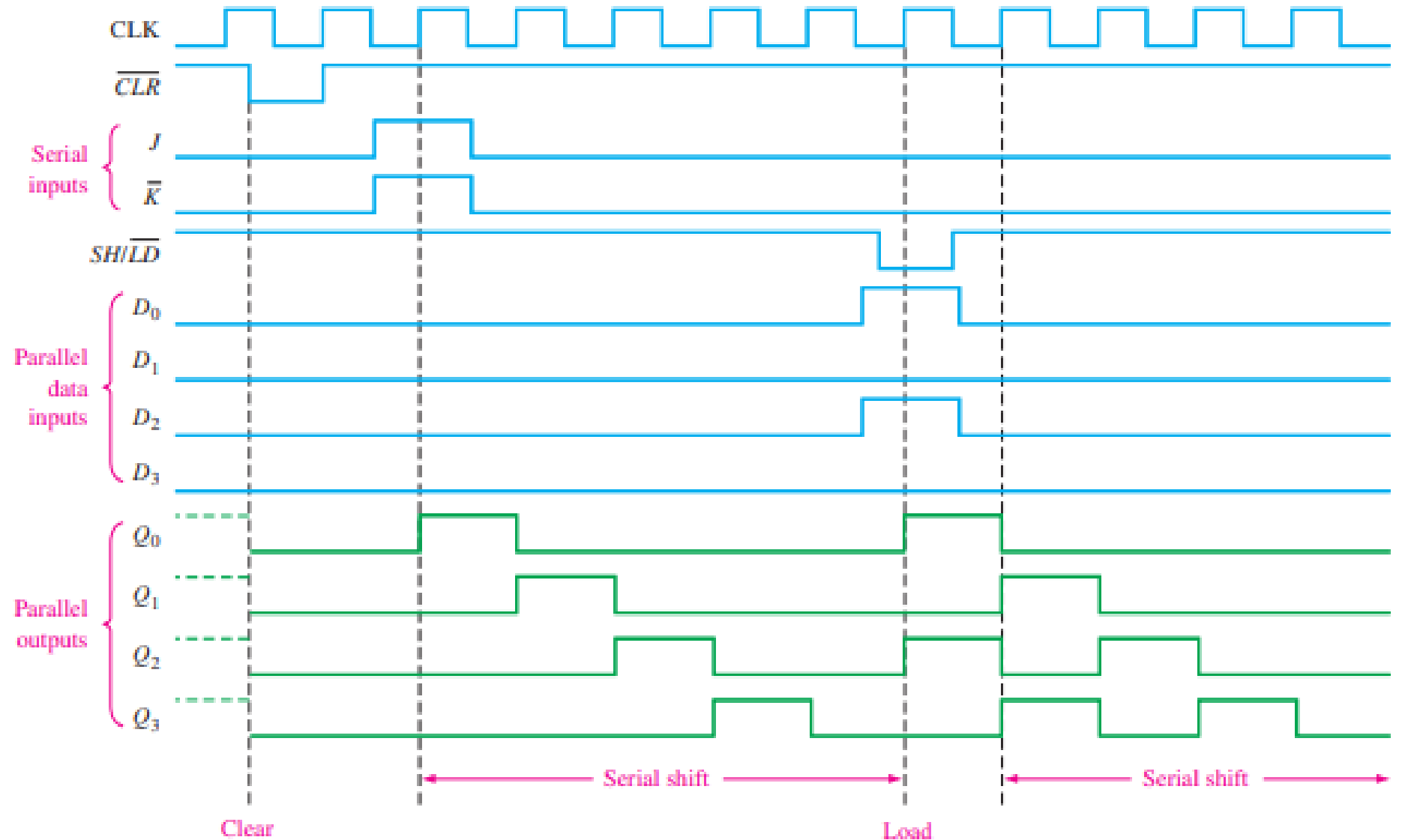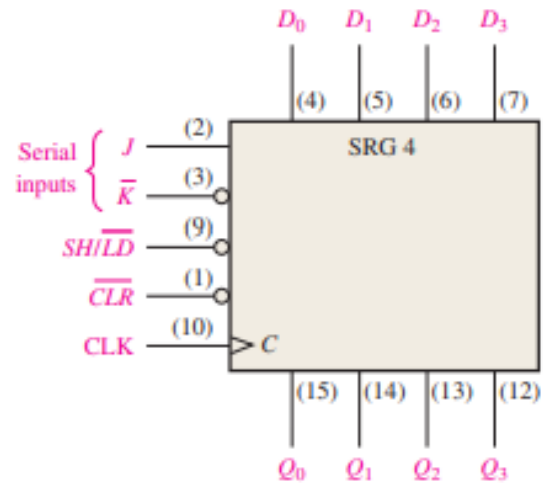Timing diagram for a 74HC195 shift register




Bidirectional shift register

- ❑ A **bidirectional** shift register is one in which the data can be shifted either left or right. It can be implemented by using gating logic that enables the transfer of a data bit from one stage to the next stage to the right or to the left, depending on the level of a control line.

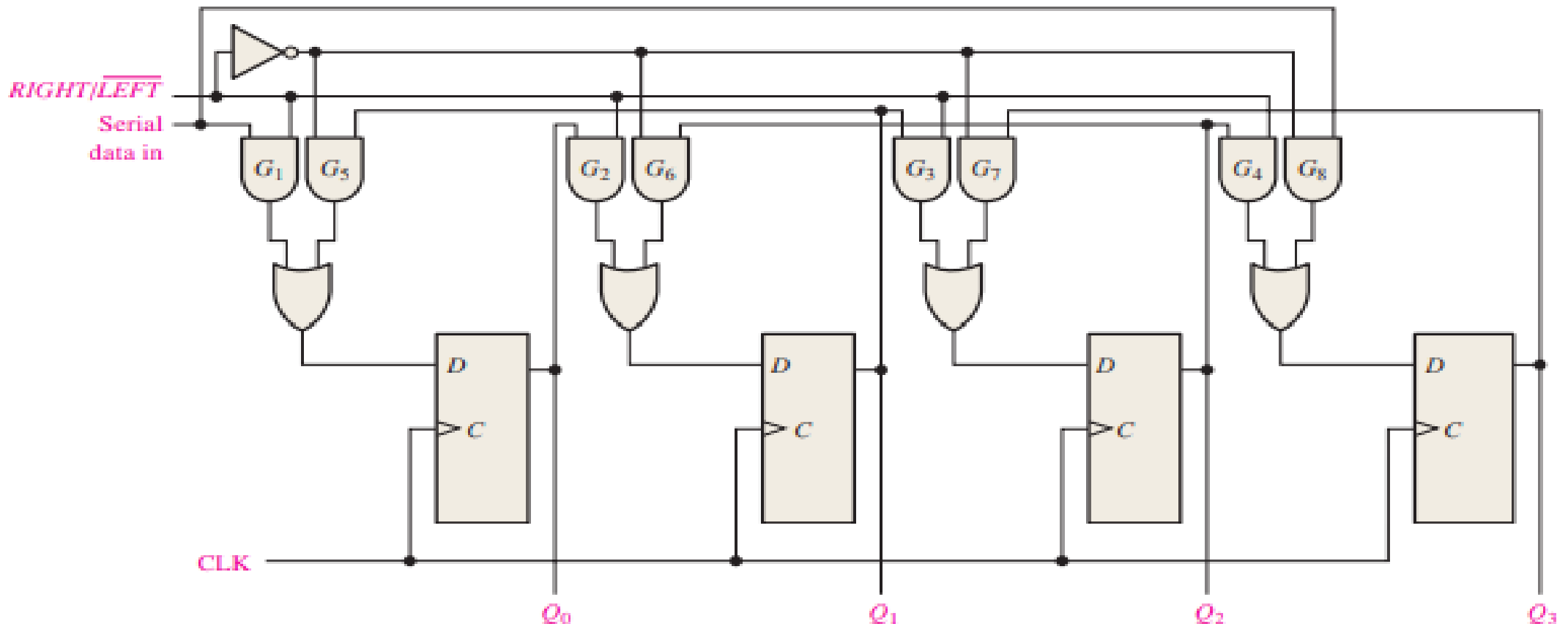


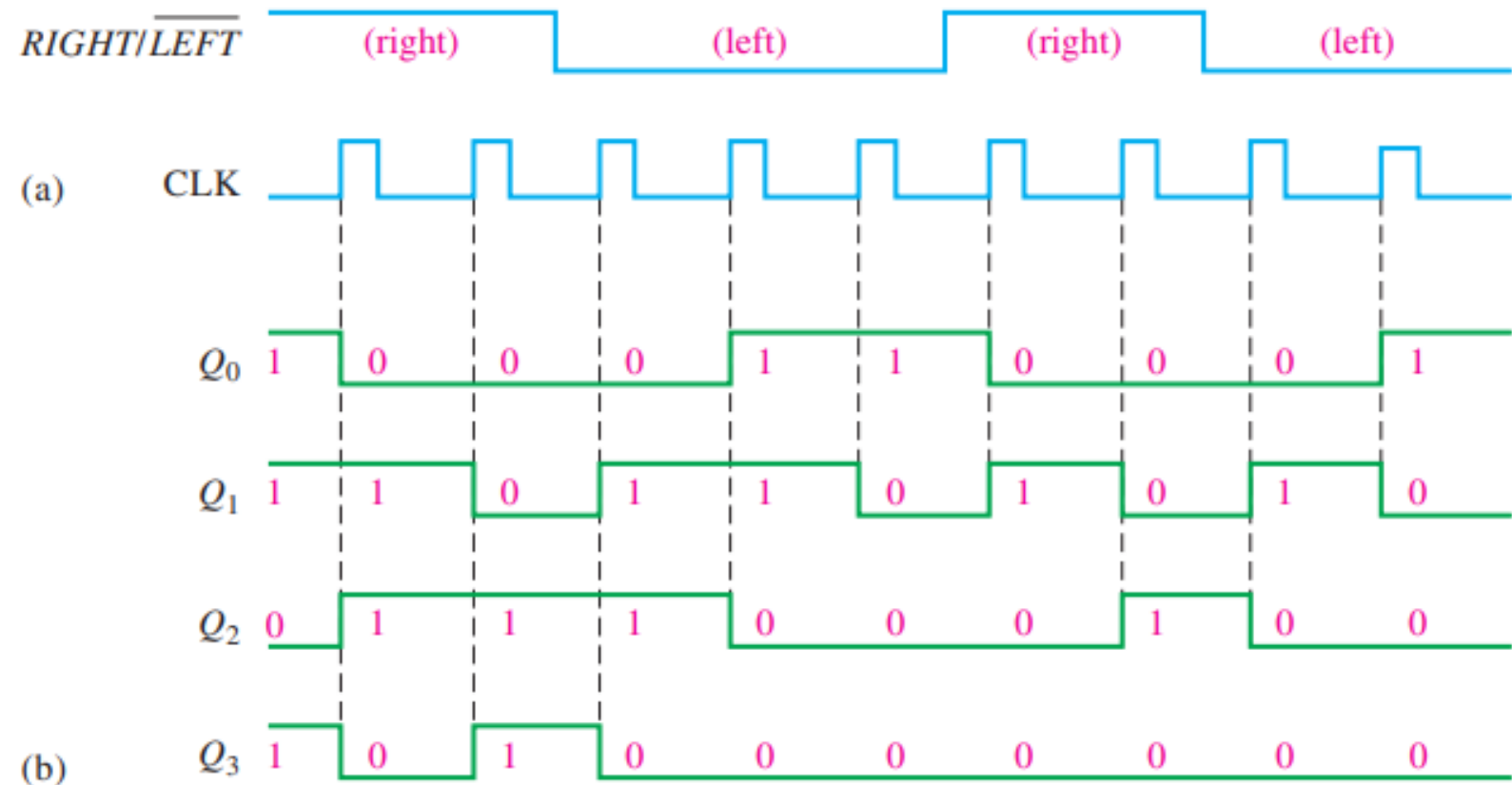EXAMPLE 8-4


Determine the state of the shift register of Figure 8-17 after each clock pulse for the given $RIGHT/\overline{LEFT}$ control input waveform in Figure 8-18(a). Assume that $Q_0 = 1$, $Q_1 = 1$, $Q_2 = 0$, and $Q_3 = 1$ and that the serial data-input line is LOW.



 Shift register application – Johnson counter



(a) Four-bit Johnson counter

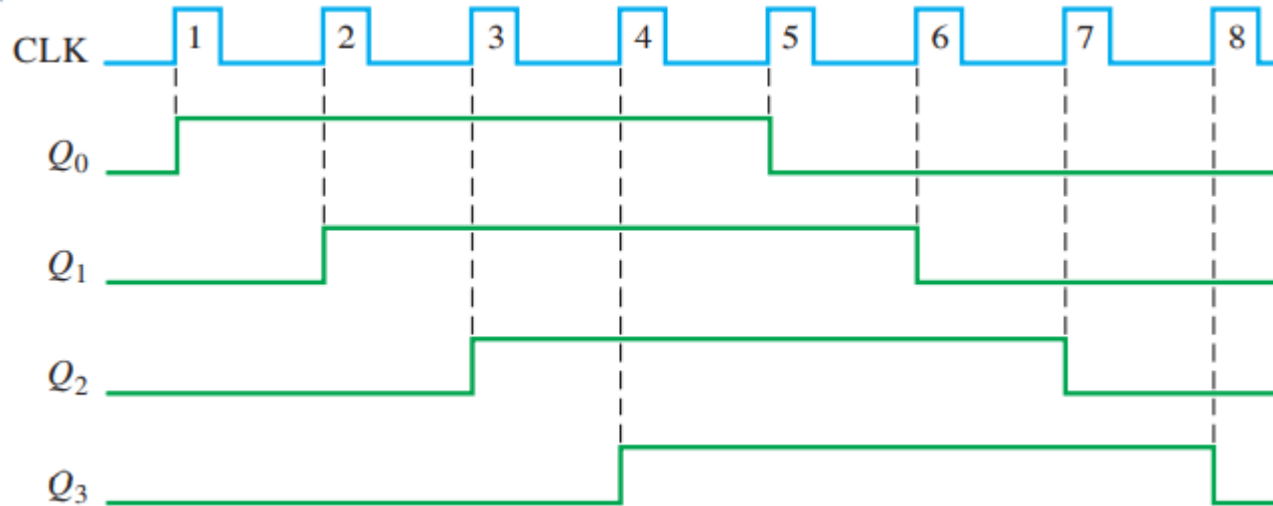


Four-bit Johnson sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1




 Shift register application – Johnson counter



Five-bit Johnson sequence.

(b) Five-bit Johnson counter

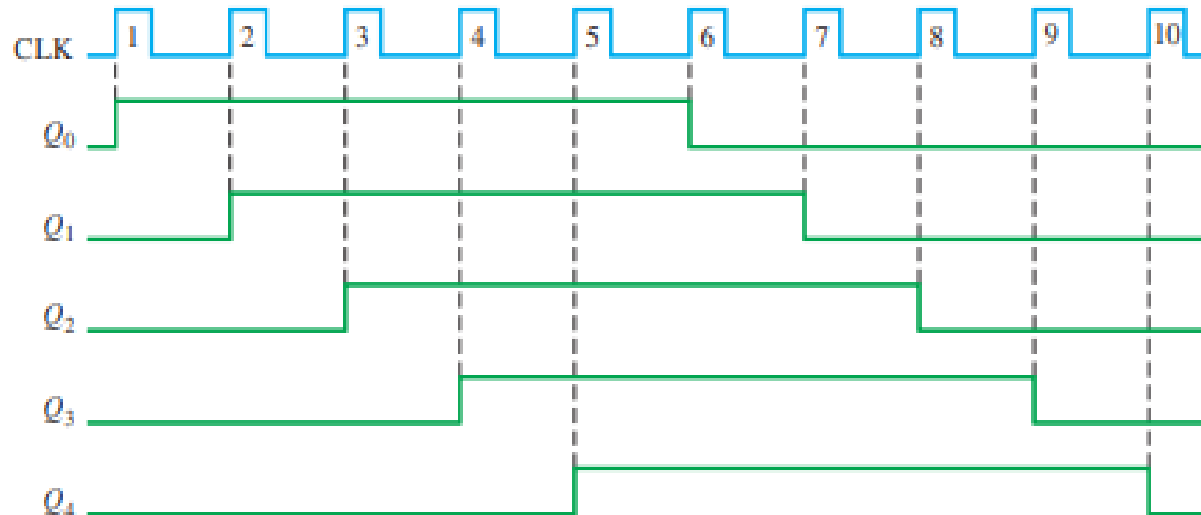


Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4
0	0	0	0	0	0
1	1	0	0	0	0
2	1	1	0	0	0
3	1	1	1	0	0
4	1	1	1	1	0
5	1	1	1	1	1
6	0	1	1	1	1
7	0	0	1	1	1
8	0	0	0	1	1
9	0	0	0	0	1



Shift register application – ring counter

- Initially, a 1 is preset into the first flip-flop, and the rest of the flip-flops are cleared.
- The ten outputs of the counter indicate directly the decimal count of the clock pulse. For instance, a 1 on Q0 represents a zero, a 1 on Q1 represents a one, a 1 on Q2 represents a two, a 1 on Q3 represents a three, and so on. You should verify for yourself that the 1 is always retained in the counter and simply shifted “around the ring,” advancing one stage for each clock pulse.

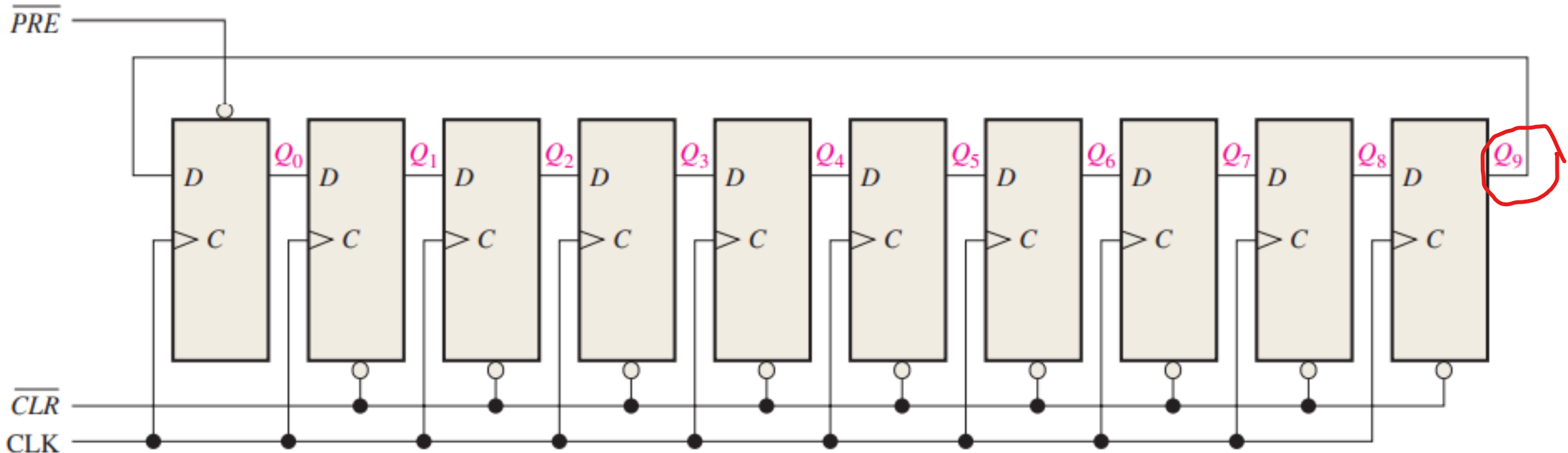



Shift register application – ring counter


Ten-bit ring counter sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7	Q_8	Q_9
0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	0	0	0	0
3	0	0	0	1	0	0	0	0	0	0
4	0	0	0	0	1	0	0	0	0	0
5	0	0	0	0	0	1	0	0	0	0
6	0	0	0	0	0	0	1	0	0	0
7	0	0	0	0	0	0	0	1	0	0
8	0	0	0	0	0	0	0	0	1	0
9	0	0	0	0	0	0	0	0	0	1



Shift register application – Johnson counter

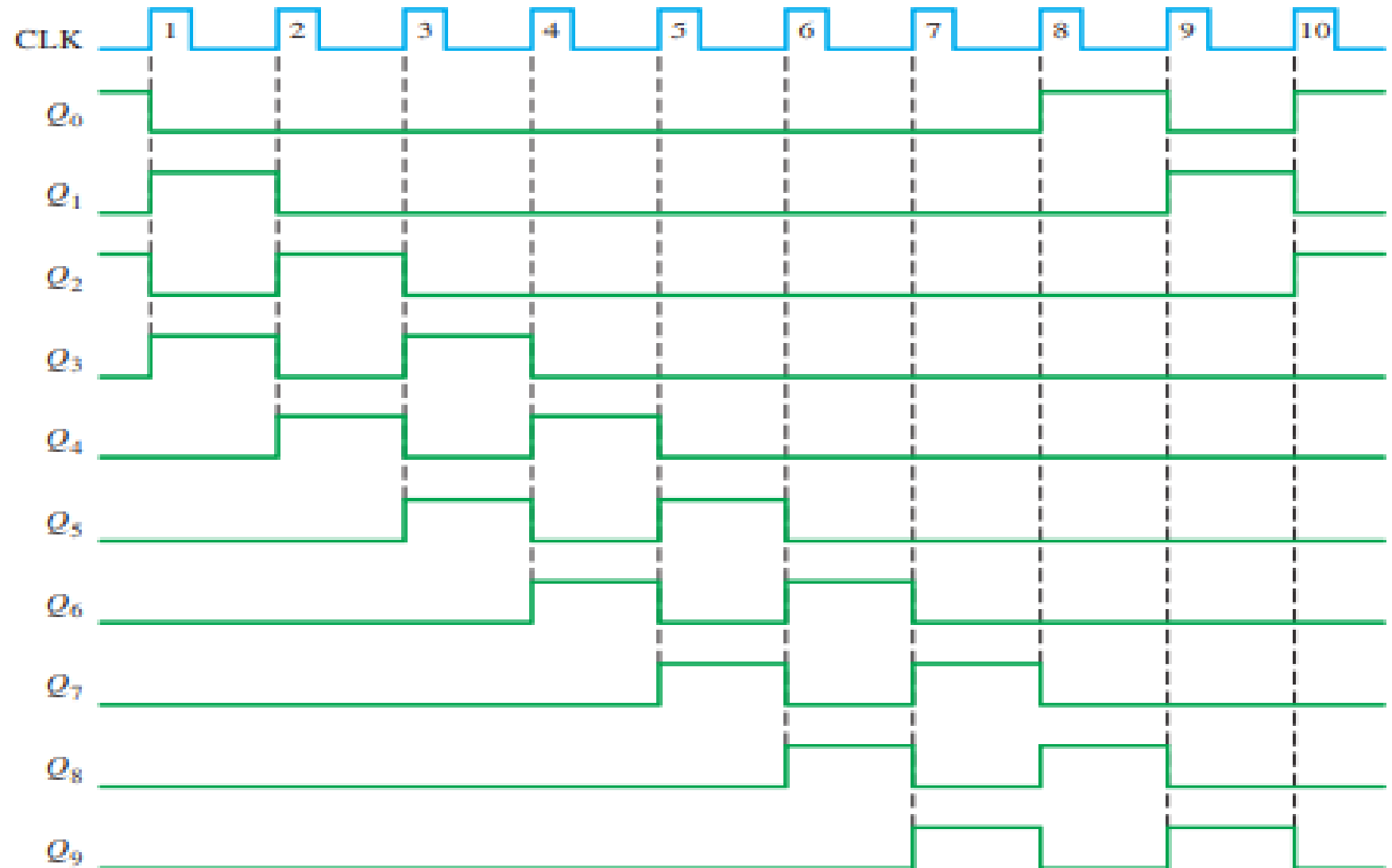PROB. If a 10-bit ring counter has the initial state 1010000000, determine the waveform for each of the Q outputs.



Shift register application – time delay


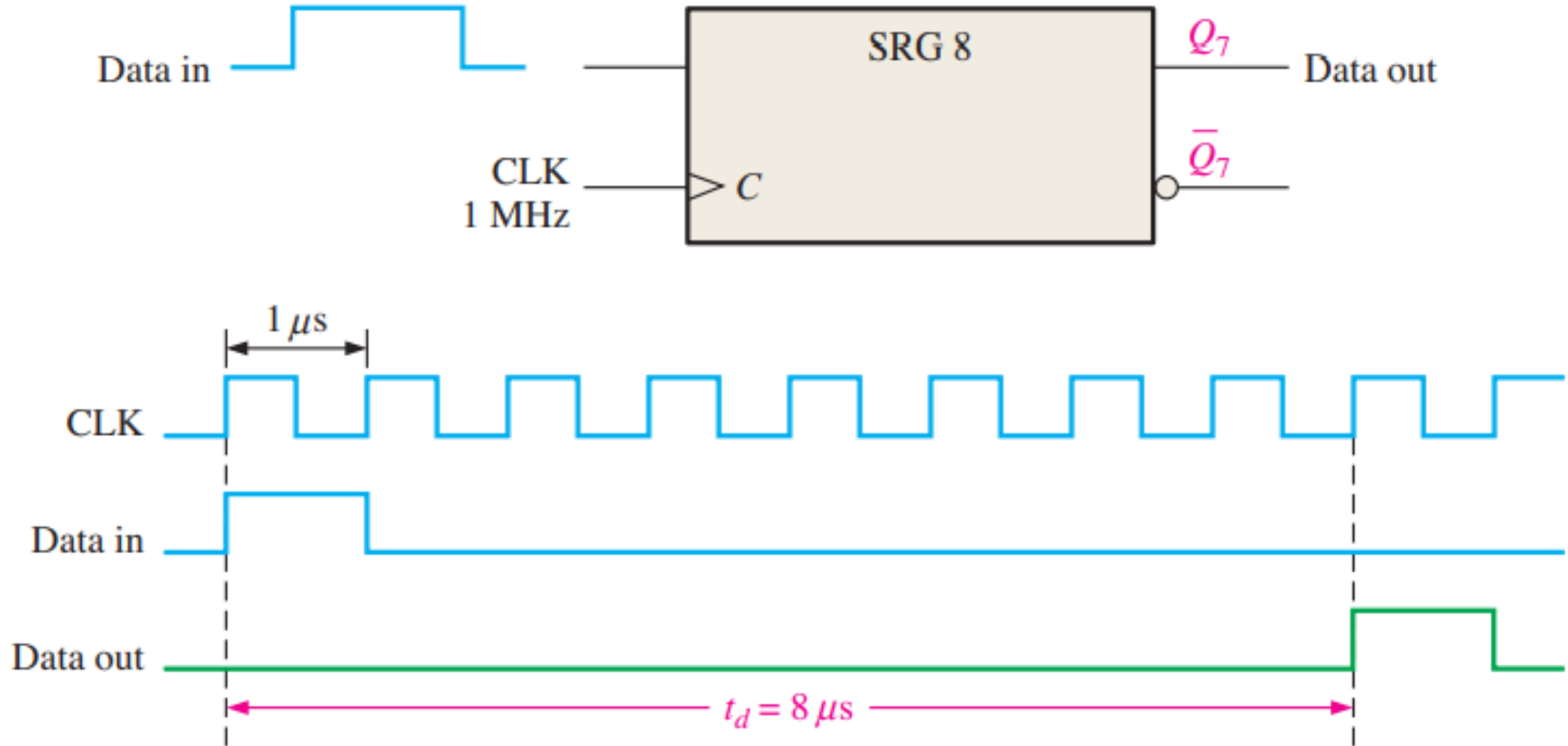


FIGURE 8-26 The shift register as a time-delay device.

Shift register application – time delay

 EXAMPLE 8-6

Determine the amount of time delay between the serial input and each output in Figure 8-27. Show a timing diagram to illustrate.




* Data shifts from Q_0 toward Q_7 .

FIGURE 8-27

Solution

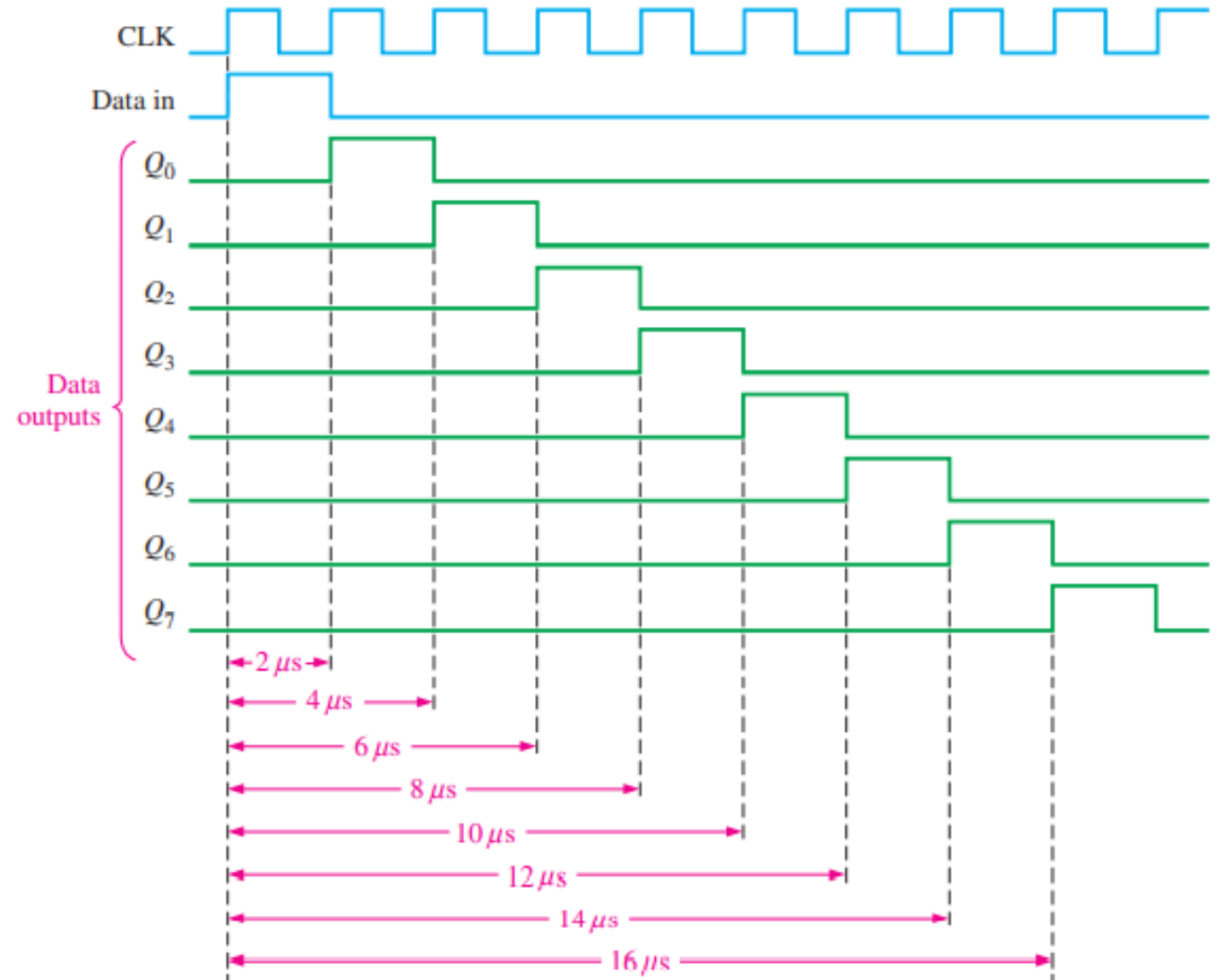The clock period is $2\ \mu\text{s}$. Thus, the time delay can be increased or decreased in $2\ \mu\text{s}$ increments from a minimum of $2\ \mu\text{s}$ to a maximum of $16\ \mu\text{s}$, as illustrated in Figure 8-28.





References

1. ***Digital Fundamentals*** by Thomas Floyd, Pearson International Edition, 11th Edition, Chapter 8, Page 449-495.



Next class



Counters